

- Q.30 Explain the use of NOR gate as universal gate.
 Q.31 Explain ramp type A/D converter.
 Q.32 Differentiate between RAM and ROM.
 Q.33 Explain the Flag register of 8085.
 Q.34 Explain the stack operation of 8085.
 Q.35 Explain briefly the 8259 PIC.

Section-D

Note: Long answer questions. Attempt any two question out of three Questions. (2x10=20)

- Q.36 With a neat sketch explain the working of Binary weighted resistor D/A converter.
 Q.37 Minimize using k-map and implement using NAND gates

$$f(A,B,C,D) = \sum(0,2,4,5,10,15) + \sum d(7,8,13,14)$$

- Q.38 With a neat sketch explain the block diagram of 8085.

Note : Course Outcome (CO) mentioned in the question paper is for official purpose only.

No. of Printed Pages : 4

120955/030955/105855

Roll No.

**5th Sem., Branch : Elect., GE, Power Station Engg.
 Subject : Digital Electronics & Microprocessors**

Time : 3 Hrs.

M.M : 100

SECTION-A

Note: Multiple type Questions. All Questions are compulsory. (10x1=10)

- Q.1 The gate whose output is 0 when the two of its inputs are 1 and 0 is
 a) AND b) Or
 c) NAND d) All of the above
- Q.2 A half adder can be constructed using a EX-OR gate and _____ gate
 a) NOR b) OR
 c) AND d) NAND
- Q.3 $A + 1 =$ _____.
 a) 0 b) 1
 c) A d) \bar{A}
- Q.4 Combining of 8 elements in a K-map results in reduction of _____ variables from o/p
 a) 1 b) 2
 c) 3 d) 4

- Q.5 Clock frequency of 8085 is
 a) 1 MHz b) 2 MHz
 c) 3 MHz d) 4 MHz
- Q.6 Full form of SOD is
 a) Semi Output Delay b) Serial Output Delay
 c) Semi Output Data d) Serial Output Data
- Q.7 Binary equivalent of 10 is
 a) 1101 b) 1010
 c) 1110 d) 1111
- Q.8 1s, Compliment representation of -8 is
 a) 00001000 b) 00000111
 c) 11111000 d) 11110111
- Q.9 Vectored address of TRAP is
 a) 0024 b) 002C
 c) 0034 d) 003C
- Q.10 Interrupt with the highest priority is
 a) INTR b) RST 6.5
 c) RST 5.5 d) TRAP

Section-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Full adder has 3 inputs (True/False)

- Q.12 Ex-Nor gate is a universal gate (True/False)
- Q.13 Draw the symbol of NAND Gate.
- Q.14 $(ABCD)_{16} = (?)_{10}$
- Q.15 $A+0=0$ (True/False)
- Q.16 $A + \bar{A} = 0$ (True/False)
- Q.17 2:1 Mux has _____ select lines.
- Q.18 Explain the use of Ready pin.
- Q.19 8085 is _____ bit microprocessor.
- Q.20 Full form of SOP is _____.

Section-C

Note: Short answer type Question. Attempt any twelve questions out of fifteen Questions. (12x5=60)

- Q.21 $(111)_8 = (?)_{10} = (?)_{16}$
- Q.22 Explain demorgans first theorem.
- Q.23 Explain the working of 8:1 MUX.
- Q.24 Explain the working of a Full Adder.
- Q.25 Differentiate between encoder and decoder.
- Q.26 Minimize using Boolean algebra
 $f(A,B,C,D) = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + A\bar{B}CD + ABCD$
- Q.27 Draw the truth table of RS Flip flap.
- Q.28 Differentiate between SOP and POS.
- Q.29 Explain 1:2 DEMUX.