

No. of Printed Pages : 4

Roll No.

220933

3rd Sem. / Electrical

Subject : Analog & Digital Electronics

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The number of valence electrons in trivalent impurity are (CO-1)

- a) 6 b) 5
- c) 4 d) 3

Q.2 A JFET is a _____ device. (CO-2)

- a) Unipolar b) Bipolar
- c) Both a and b d) None of the above

Q.3 What is the rectifier's efficiency of half wave? (CO-2)

- a) 40% b) 40.6%
- c) 81% d) 81.6%

(1)

220933

Q.4 An inverter is also called as _____ gate. (CO-3)

- a) NAND b) NOT
- c) NOR d) AND

Q.5 The basic storage element in digital systems is (CO-4)

- a) Counter b) Encoder
- c) Flip Flop d) Mux

Q.6 The number of select lines for 1:16 DEMUX are (CO-4)

- a) 1 b) 4
- c) 2 d) 3

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 PIV stands for _____ (CO-1)

Q.8 MOSFET stands for _____ (CO-2)

Q.9 Draw symbol of npn transistor. (CO-2)

Q.10 10110-10010 = _____ (CO-3)

(2)

220933

- Q.11 The modulus of 4 bit binary counter is _____
(CO-4)
- Q.12 SIPO stands for _____ (CO-4)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Discuss effect of temperature on the conductivity of intrinsic semiconductors. (CO-1)
- Q.14 Draw and explain v-I characteristics of a pn junction diode. (CO-1)
- Q.15 Explain how a shunt capacitor removes the ripple. (CO-1)
- Q.16 Give the input and output characteristics of transistor in CB configuration. (CO-2)
- Q.17 Differentiate between BJT and JFET. (CO-2)
- Q.18 Do the following conversions (CO-3)
- $(75)_8 = (?)_2$
 - $(1C2)_{16} = (?)_{10}$
- Q.19 Explain AND gate with truth table. (CO-3)

(3)

220933

- Q.20 Discuss about half adder circuit. (CO-4)
- Q.21 Write a short note on 1:8 DE-MUX. (CO-4)
- Q.22 Write a short note on RS FF. (CO-4)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Define a rectifier. Discuss about the types of rectifier. Explain any one in detail. (CO-1)
- Q.24 Explain in detail working of 4 bit synchronous / asynchronous counter. (CO-4)
- Q.25 Write short note on the following.
- Transistor as an amplifier in CE configuration. (CO-2)
 - NOR gate as universal gate. (CO-3)

(**Note:** Course outcome/CO is for office use only)

(2080)

(4)

220933