

No. of Printed Pages : 4  
Roll No. ....

170927

**2nd Sem / Electrical Engg**  
**Subject:- Electronics - I**

Time : 3Hrs.

M.M. : 100

**SECTION-A**

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 What is rectification? (CO1)
- a) Process of conversion of ac into dc
  - b) Process of conversion of low ac into high ac
  - c) Process of conversion of dc into ac
  - d) any of the above
- Q.2 Potential barrier for Ge Diode is ? (CO1)
- a) 0.3                                      b) 0.7
  - c) 1.0                                      d) 1.3
- Q.3 Efficiency of half wave rectifier is (CO1)
- a) 40.6%                                      b) 70.4%
  - c) 81.2%                                      d) 50%
- Q.4 What are the charge carriers in semiconductors ? (CO1)
- a) Electrons and holes    b) Electrons
  - c) Holes                                      d) Charges
- Q.5 Identify the relationship between base current amplification (  $\beta$  ) and emitter current amplification (  $\alpha$  ). (CO2)
- a)  $\alpha = \beta / 1 + \beta$                                       b)  $\beta = \alpha / 1 - \alpha$

(1)

170927

- c)  $\alpha = \beta / 1 + \beta$                                       d)  $\beta = \alpha / 1 - \alpha$
- Q.6 Which region of the transistor is lightly doped? (CO2)
- a) Emitter
  - b) Base
  - c) Collector
  - d) Both Emitter and Collector
- Q.7 The maximum output amplified signal is obtained when the operating point of the transistor is (CO3)
- a) near saturation
  - b) in the middle of the active region
  - c) near cutoff region
  - d) any of the above
- Q.8 The voltage gain is practically expressed in \_\_\_\_\_ (CO4)
- a) db    b) volts
  - c) as a number                                      d) ampere
- Q.9 What is Amplification factor in FET? (CO6)
- a) Ratio of change in drain to source voltage to change in gate to source voltage
  - b) Ratio of change in drain current to change in gate to source voltage
  - c) Ratio of change in collector current to change in drain current
  - d) Ratio of change in collector current to change in gate to source voltage
- Q.10 Comparing the size of BJT and FET, choose the correct statement ? (CO6)

(2)

170927

- a) BJT is larger than the FET
- b) BJT is smaller than the FET
- c) Both are of same size
- d) Depends on application

### SECTION-B

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What is Drift current. (CO1)
- Q.12 Tell maximum rectification efficiency of a half wave rectifier. (CO1)
- Q.13 A single stage amplifier contains \_\_\_\_\_ transistors. (CO3)
- Q.14 Define Ripple factor. (CO1)
- Q.15 Draw a symbol of NPN transistor. (CO2)
- Q.16 What is Quiescent point. (CO3)
- Q.17 What is Voltage gain. (CO4)
- Q.18 Define multistage transistor Amplifier. (CO5)
- Q.19 Write the full form of MOSFET. (CO6)
- Q.20 Draw the symbol of LED. (CO1)

### SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Draw the V/I characteristics of PN junction Diode and explain it. (CO1)
- Q.22 What are filter circuits. Explain its need. (CO1)
- Q.23 Explain the working of PNP transistor. (CO2)
- Q.24 Explain the effect of temperature on the operating point of a transistor. (CO3)
- Q.25 Draw and explain DC Load line. (CO4)

(3)

170927

- Q.26 Explain the need of stabilization of operating point. (CO3)
- Q.27 Discuss transformer couplings used in multi stage transistor amplifier. (CO5)
- Q.28 Explain potential divider biasing circuit. (CO3)
- Q.29 Draw the characteristics of zener diode and explain it (CO1)
- Q.30 Explain the concept of h-parameters of a transistor. (CO3)
- Q.31 Draw the circuit of 2-stage RC coupled transistor amplifier. (CO5)
- Q.32 What are the main advantages of FET over BJT. (CO6)
- Q.33 Draw the AC equivalent circuit of single stage amplifiers. (CO4)
- Q.34 Draw and explain Emitter follower circuit. (CO5)
- Q.35 Explain the working of N channel JFET. (CO6)

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Draw the circuit diagram of Full wave rectifier bridge and explain its working along with waveforms. (CO1)
- Q.37 Compare all the three configurations of Transistors in detail. (CO2)
- Q.38 Draw the circuit of single stage transistor amplifier and explain it. (CO3)

(**Note:** Course outcome/CO is for office use only)

(1080)

(4)

170927