

Roll no. _____

ID: 180945/170945

Semester: 4th

Branch: Electrical

Subject Name: Digital Electronics

Time Allowed : 3 Hrs.

MM:100

Section –A

Note: Multiple Choice questions. All questions are compulsory.

10x1=10

- Q.1 How many nibbles are there in 10011110 number
a. 3 b. 4
c. 2 d. 8
- Q.2 According to commutative law of addition
a. $ABC = (AB) C$ b. $B=B+B$
c. $A+B = B+A$ d. None of these
- Q.3 On a K-map, grouping of 1's produces
a. SOP expression b. POS expression
c. AND-OR logic d. None of these
- Q.4 Which logic circuit has a memory
a. Combinational Logic Circuit b. Sequential Logic Circuit
c. Both d. None
- Q.5 For D = 0 flip flop responds to
a. Set b. Reset
c. No Change d. Toggle
- Q.6 A Decimal to BCD Encoder is also known as:
a. 4-line-to-10-line encoder b. 4-line-to-16-line encoder
c. 10-line-to-4-line encoder d. 16-line-to-4-line encoder
- Q.7 A 8 : 1 MUX has Select lines
a. 8 b. 3
c. 2 d. 4
- Q.8 The inverter is.....
a. NAND b. OR
c. AND d. NOT
- Q.9 Which gate is known as universal gate?
a. AND b. NAND
c. XOR d. XNOR
- Q.10 The radix of an Octal Number System is.....
a. 8 b. 7
c. 6 d. 9

Section-B

Note: Objective type questions. All questions are compulsory.

10x1=10

- Q.11 Define term K-MAP.
- Q.12 What is Logic Gate?
- Q.13 Write any two applications of A/D converters.
- Q.14 Name different types of Shift Registers.
- Q.15 Define Min term.
- Q.16. Prove that $A + A.B = A$
- Q.17 Draw the symbol of EX-OR gate
- Q.18 What is Counter?
- Q.19 Define Analog Signal.
- Q.20 Write full form of ASCII and EBCDIC.

Section –C

Note: Short answer type Questions. Attempt any twelve questions out of fifteen questions.

12x5=60

- Q.21 What do you mean by Digital Signal? Explain advantages and application of Digital signal.

- Q.22 Multiply the following Binary Numbers:
 (i) 110110×0110 (ii) 10101×101
- Q.23 What is Error Correcting Code? How it can be corrected by using parity?
- Q.24 Do the subtraction by using 2's complement method of subtraction:
 (i) $1001 - 1110$ (ii) $11011 - 01101$
- Q.25 Explain Block diagram, Logical expression, Truth Table of Decimal to BCD Encoder.
- Q.26 Design Block diagram, Truth Table, Logical Expression of 8 : 1 MUX.
- Q.27 Differentiate between Synchronous Counter and Asynchronous Counter
- Q.28 Draw the symbol, logical expression, truth table and pulse operation of EX-NOR gate.
- Q.29 Solve the following Boolean expression:
 (i) $ABC + AB\bar{C}D + AB\bar{C} + A\bar{B}D + A\bar{D}$
 (ii) $XY + X(Y+Z) + Y(Y+Z)$
- Q.30 State and explain Demorgan's Theorems.
- Q.31 Why NAND and NOR gates are known as universal gates?.
- Q.32 Explain the working of PIPO shift register with the help of pulse diagram.
- Q.33 Discuss truth table, logic diagram and logical expression of a Full Adder.
- Q.34 What do you mean by DEMUX? Design a 1 : 8 DEMUX by using truth table, logical expression and logical circuit.
- Q.35 What is the difference between Latch and Flip-Flop?

Section-D

Note: Long answer questions. Attempt any two questions out of three questions.

2x10=20

- Q.36 Minimize the following Boolean expression using K-Map and realize the logic Circuit using NAND gates only.
 $F(A,B,C,D) = \sum M(1,3,5,7,9,15) + d(4,6,12,13)$
- Q.37 Explain the Logic Diagram, Truth Table and Operation of a J-K flip flop with neat Diagram.
- Q.38 Write short note on following:
 a. Binary Weighted Digital to Analog Converter
 b. Ring Counter