

No. of Printed Pages : 4

181035

Roll No. ....

3rd Sem / Eltx

**Subject:- Network Filters and Transmission Lines**

Time : 3Hrs.

M.M. : 100

### SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

Q.1 If an asymmetrical network is terminated by an impedance such that its input impedance is equal to its terminating impedance, then such impedance is called: (CO1)

- a) Source impedance    b) Load impedance  
c) Iterative impedance    d) Image impedance

Q.2 Attenuation in any symmetrical attenuator is given by (CO3)

- a)  $a = 20 \log \sqrt{\frac{R_1}{R_2}}$     b)  $a = 20 \log \sqrt{\frac{I_1}{I_2}}$   
c)  $a = 20 \log \frac{I_1}{I_2}$     d)  $a = 10 \log \frac{I_1}{I_2}$

Q.3 An attenuator consist of (CO3)

- a) Only resistors  
b) Only capacitors  
c) Only inductors  
d) Both resistor and inductors

Q.4 In a prototype high pass filter p- section, characteristics impedance is maximum at which frequency? (CO5)

- a) Zero    b)  $f_c$   
c)  $1.5f_c$     d) Infinity

Q.5 A filter having two inductor in series arm and a capacitor in shunt arm is a (CO5)

- a) LPF    b) HPF  
c) BPF    d) BSF

Q.6 In a m-derived terminating half section value of m is (CO5)

- a) 0    b) 0.3  
c) 0.6    d) 0.9

Q.7 Reflection coefficient of a line terminated in its characteristic impedance is (CO7)

- a) -1    b) 0  
c) 1    d) Infinity

Q.8 A finite length transmission line behaves as infinite long line when the load end is (CO7)

- a) Open circuited  
b) Short circuited  
c) Terminated by its characteristic impedance  
d) Terminated by an impedance other than characteristic impedance

Q.9 For a short circuited line load current maxima occurs at (CO7)

- a) Load  
b) Source  
c) At midpoint of load and source  
d) At any point between load and source

Q.10 If  $k=0$ , then VSWR will be (CO7)

- a) 0    b) 1  
c) -1    d) Infinity

### SECTION-B

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Draw a symmetrical lattice network (CO1)
- Q.12 Define short circuit impedance (CO1)
- Q.13 Define iterative transfer constant (CO1)
- Q.14 Define image impedance (CO1)
- Q.15 1 Neper = \_\_\_\_\_ dB. (CO2)
- Q.16 L-Type attenuator is a form of symmetrical attenuator (True/False) (CO3)
- Q.17 Draw a m-derived T-section low pass filter (CO5)
- Q.18 Condition for a distortion less line is \_\_\_\_\_ (CO7)
- Q.19 Draw the equivalent circuit of a transmission line (CO7)
- Q.20 Distance between successive voltage maxima is \_\_\_\_\_ (CO7)

### SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Differentiate between unilateral and bilateral network. (CO1)
- Q.22 Explain propagation constant of a symmetrical network. (CO1)
- Q.23 Explain briefly insertion loss. (CO1)
- Q.24 Obtain a half section by splitting a T-network. (CO1)
- Q.25 Distinguish between balanced and unbalanced attenuator. (CO3)
- Q.26 List five applications of attenuators. (CO3)

(3)

181035

- Q.27 List two disadvantages of prototype filter (CO2)
- Q.28 Compare active and passive filters (CO4)
- Q.29 Design a constant-k low pass filter p section having cutoff frequency 3KHZ and characteristics impedance 600Ω. (CO5)
- Q.30 Explain the construction and working of double crystal BPF. (CO8)
- Q.31 Explain briefly the secondary constant of a transmission line. (CO7)
- Q.32 Explain the causes of distortion in a transmission line. How can this be minimized (CO7)
- Q.33 Explain stub matching (CO7)
- Q.34 List two advantages and two disadvantages of HVDC (CO9)
- Q.35 Give five applications of transmission line (CO7)

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Design a p- type attenuator to give 20 dB attenuation, having a characteristics impedance of 100 Ω (CO3)
- Q.37 Explain the need of Filters, with a neat gain vs freq plot explain the working of a high pass filter. Draw a T-section of m-derived high pass filter. (CO6)
- Q.38 Explain the concept of reflection and formation of standing waves in a transmission line. Draw the standing wave pattern for a short circuit line (CO7)

(1400)

(4)

181035