

No. of Printed Pages : 4  
Roll No. ....

221014/212817

**1st Sem / ECE/ Instrumentation & Control engg./  
Automation & Robotics / Medical electronics/ ECE  
For Speech and Hearing Impaired)  
Subject : Fundamental of Electrical Engineering /  
Fundamental of Electrical Engg.**

Time : 3 Hrs.

M.M. : 60

**SECTION-A**

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The unit of Resistance is \_\_\_\_\_

- a) Ohm                                      b) Ohm-meter
- c) Volt                                        d) Ampere

Q.2 1 kWh = \_\_\_\_\_

- a)  $3.6 \times 10^6 \text{ J}$                               b)  $3.6 \times 10^5 \text{ J}$
- c)  $0.36 \times 10^6 \text{ J}$                               d)  $0.36 \times 10^5 \text{ J}$

Q.3 Ammeter is used to measure \_\_\_\_\_

- a) Current                                    b) Voltage
- c) Power                                      d) Resistance

(1) 221014/212817

Q.4 In ideal current source, the internal resistance is \_\_\_\_\_

- a) Zero                                        b) One
- c) Infinite                                    d) None of the above

Q.5 MMF stands for \_\_\_\_\_

- a) Magnetic motion force
- b) Magnetomotive force
- c) Magneto material force
- d) None of the above

Q.6 Which electrolyte is used in lead acid battery?

- a)  $\text{H}_2\text{SO}_4$                                     b)  $\text{Ag}_2\text{O}$
- c)  $\text{MnO}_2$                                      d) None of the above

**SECTION-B**

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 The frequency of AC power supply in India is \_\_\_\_\_

Q.8 The resistance of wires is inversely proportional to its length (True/False)

(2) 221014/212817

- Q.9 Draw the symbol of battery.
- Q.10 In maximum power transfer theorem, the load resistance is equal to the source resistance (True/False)
- Q.11 Write the unit of flux.
- Q.12 Define secondary cell.

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 List the factors affecting resistance of a conductor.
- Q.14 Derive an expression of equivalent capacitance when capacitors connected in parallel.
- Q.15 Describe ohm's law.
- Q.16 Write a short note on Kirchhoff's current law.
- Q.17 Define form factor and peak factor.
- Q.18 Define constant voltage source and current source. Draw their characteristics.
- Q.19 Differentiate between AC and DC.
- Q.20 Explain Faraday's law of electromagnetic induction.
- Q.21 Calculate power in pure resistance circuit.

- Q.22 Explain analogy between electric and magnetic circuit.

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Derive an expression of star to delta conversion.
- Q.24 Describe construction and working principle of Lead acid battery.
- Q.25 Write a short note on :
- Solar cell.
  - Thevenin's theorem