

No. of Printed Pages : 4
Roll No.

220914

1st Sem. / Electrical

Subject : Principles of Electrical Engineering

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 Unit of current is (CO1)
a) Farad b) Volts
c) Ampere d) Coulomb
- Q.2 Unit of Capacitance is (CO1)
a) Farad b) Coulomb
c) Volt d) Ohm
- Q.3 Power is measured by (CO1)
a) Ammeter b) Wattmeter
c) Energy meter d) Voltmeter
- Q.4 An ideal current source has internal resistance (CO2)
a) Zero b) One
c) Two d) Infinity
- Q.5 Unit of M.M.F is (CO3)
a) Ampere b) Ampere turns
c) Farad d) Joule

(1)

220914

Q.6 In Lead acid cell the Negative plate is made of (CO5)

- a) Lead oxide b) Iron
c) Zinc d) Lead

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 Unit of Energy is (CO1)
- Q.8 Property which opposes flow of electric current in a conductor is called _____ (CO1)
- Q.9 Unit of Flux is _____. (CO3)
- Q.10 As the frequency increases, Eddy current loss Increases/ Decreases. (CO4)
- Q.11 Two parallel current carrying conductors experience _____. (CO3)
- Q.12 Capacity of Battery is in Ampere X _____. (CO5)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Explain the factors affecting Capacitance of a capacitor. (CO1)
- Q.14 State and explain Ohm's Law. (CO2)
- Q.15 Two resistance of 3 Ω and 6 Ω are first connected in series and then in parallel. Find the total Resistance in each case. (CO2)
- Q.16 Define and explain Kirchoff's voltage law. (CO2)

(2)

220914

- Q.17 Explain similarity between Electric circuit & Magnetic circuit. (CO3)
- Q.18 Explain the concept of self Inductance. (CO4)
- Q.19 Explain various methods of charging of lead Acid battery. (CO5)
- Q.20 Three Resistance of 6Ω , 12Ω and 18Ω are connected in Delta. Convert it into equivalent Star.
- Q.21 Derive the expression for Energy stored in an Inductor. (CO4)
- Q.22 Explain effect of Temperature on the Resistance of Conductor. (CO1)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain construction, Working principle and applications of Lead Acid Battery or Lithium ion Battery. (CO5)
- Q.24 Explain Concept of voltage source, current source, connections and their conversions. (CO2)
- Q.25 Write short note on any two.
- a) Hysteresis Loss (CO4)
 - b) Kirchhoff's current Law (CO2)
 - c) Capacitors in Series and Parallel. (CO1)