

No. of Printed Pages : 4                      180832/170832/120832  
Roll No. ....                                      /030832/031034/106544

**3rd Sem / Comp, IT, Eltx, EI, Med. Eltx., Power Eltx,  
Elect. & Eltx. Engg.**

**Subject:-Digital Electronics/ Digital Eltx. - I**

Time : 3Hrs.

M.M. : 100

### SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 NOT gate has \_\_\_\_\_ output.  
a) 1                                      b) 2  
c) 3                                      d) 4
- Q.2 Base/Radix of Hexadecimal number system is \_\_\_\_\_.  
a) 16                                      b) 8  
c) 2                                      d) 10
- Q.3 Output of EX-NOR gate is \_\_\_\_\_ when both of its inputs are HIGH.  
a) 1                                      b) 0  
c) invalid                                      d) None of the above
- Q.4 A quad group in K-maps eliminates \_\_\_\_\_ number of variables.  
a) 2                                      b) 4  
c) 3                                      d) 1

(1) 180832/170832/120832  
/030832/031034/106544

- Q.5 A full adder has \_\_\_\_\_ inputs.  
a) 2                                      b) 3  
c) 4                                      d) 5
- Q.6 A 1:8 demultiplexer has \_\_\_\_\_ select lines.  
a) 2                                      b) 3  
c) 4                                      d) 8
- Q.7 An encoder is a \_\_\_\_\_ circuit.  
a) Sequential                                      b) Combinational  
c) Both (a) and (b)                                      d) None of the above
- Q.8 If S=1 & R=1 then the output (Q) of S-R flip flop is \_\_\_\_\_.  
a) 1                                      b) 0  
c) Invalid                                      d) None of the above
- Q.9 Decade counter has \_\_\_\_\_ states.  
a) 5                                      b) 9  
c) 4                                      d) 10
- Q.10 IC used for ALU is \_\_\_\_\_.  
a) 7408                                      b) 74266  
c) 74181                                      d) 7400

### SECTION-B

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Give any one advantage of digital signal over analog Signal.

(2) 180832/170832/120832  
/030832/031034/106544

- Q.12 Draw the symbol and truth table of EX-OR Gate.
- Q.13 State De-Morgan's Theorem.
- Q.14 Give a truth table of 4:1 multiplexer.
- Q.15 Full Form of EPROM is \_\_\_\_\_.
- Q.16 Write any one advantage of the flip flop over the latch.
- Q.17 Explain the mode number (Modulus) in the counter.
- Q.18 Expand TTL.
- Q.19 Give the IC number of 4-bit ALU.
- Q.20 Define Accuracy in DAC.

### SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Differentiate between Analog signal and digital signal.
- Q.22 Convert  $(6A8C)_{16}$  Hexadecimal number into binary number.
- Q.23 Explain 3-bit Excess-3 code and Gray code.
- Q.24 Explain the NOR gate as a universal logic gate.
- Q.25 Explain the Full adder with circuit diagram.
- Q.26 Define 8:1 multiplexer.
- Q.27 Explain Decimal to BCD Encoder.
- Q.28 Subtract 1101 from 0101 using 2's complement method of subtraction.

(3) 180832/170832/120832  
/030832/031034/106544

- Q.29 What is race around condition in J-K flip flop?
- Q.30 Differentiate between latch and flip flop.
- Q.31 What is SIPO?
- Q.32 Explain different types of ROM.
- Q.33 Explain ALU in detail.
- Q.34 Give symbol and truth table of SR- flip flop and JK - flip flop.
- Q.35 Explain successive approximation ADC.

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Simplify with the help of K-Map  $f(A,B,C,D) = \sum m(0,1,7,9,11,13,14) + \sum d(3,5,6,10,15)$  and realize the expression using NAND gates.
- Q.37 Explain R/2R ladder digital to analog converter with neat diagrams.
- Q.38 Write a short note on any two of the following:
- Ring Counter
  - Race around condition
  - D-flip flop.

(2340)

(4) 180832/170832/120832  
/030832/031034/106544