

No. of Printed Pages : 4
Roll No.

220824

**2nd Sem / Branch : Computer, Computer (For
Speech and Hearing Impaired)
Subject:- Analog Electronics**

Time : 3Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 When an Atom loses its electron, it becomes (COE1)
a) A Positive Ion
b) Becomes electrically Neutral
c) Becomes Negative Ion
d) None of these
- Q.2 Process of adding impurities in a pure semiconductor (COE1)
a) Biasing b) Potential Barrier
c) Dopping d) None of these
- Q.3 IC 555 Timer can be used as (COE4)
a) Astable Multivibrator
b) Both A&C
c) Bistable Multivibrator
d) None of these
- Q.4 A Zener Diode is used as (COE1)
a) Coupler b) An Amplifer
c) Rectifier d) Voltage Regulator

(1)

220824

- Q.5 Most commonly used transistor configuration is (COE2)
a) Common Collector b) Common Base
c) Common Emitter d) All of these
- Q.6 Transistor is used as a switch (COE2)
a) True b) False

SECTION-B

Note: Objective type questions. All questions are compulsory. (6x1=6)

- Q.7 Expand PIV (COE3)
- Q.8 What is Thermister (COE1)
- Q.9 What is Voltage Regulator (COE1)
- Q.10 Draw symbol of MOSFET (COE2)
- Q.11 What is the Function of Oscillator (COE4)
- Q.12 What do you mean by Ripples (COE3)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Draw half wave Rectifier. What is its Ripple Factor? (COE3)
- Q.14 Write down the Properties of Semiconductor. (COE1)
- Q.15 What do you mean by Thermal Runaway? (COE2)
- Q.16 Draw block diagram of regulated power supply (COE3)

(2)

220824

- Q.17 State difference between acceptor and Donar impurities. (COE1)
- Q.18 What is CMMR (COE5)
- Q.19 How transistor can work as a switch (COE2)
- Q.20 Show how PI Filter works (COE3)
- Q.21 What is the function of Opamp as integrator ? (COE5)
- Q.22 Write some features of IC 555 timer. (COE5)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.36 Explain the working of push pull amplifier. (COE4)
- Q.37 Draw and explain pin diagram of 555 timer (COE5)
- Q.38 Differentiate between BJT and MOSFET (COE2)