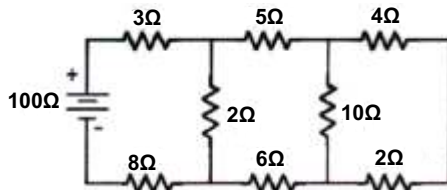


SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

Q.36 Find the current through each branch by network reduction technique.



Q.37 What are the various applications of Single Phase and Three Phase motors? Describe in detail.

Q.38 A 10 Ohm resistor is connected in series of 230 V 50 Hz supply. What is the

- Peak Voltage
- Current flowing and the power dissipated in the resistor
- If an Inductor $L=50$ mH is added to the circuit in series, what is the total impedance
- What is the current flowing in R-L circuit.
- What is the power dissipated in AC circuit?

No. of Printed Pages : 4

Roll No.

187734/147734

4th Sem / Branch : Aircraft Maintenance Engg

**Subject:- Elements of Electrical and
Electronics Engineering-I**

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

Q.1 For making measurement, an ammeter is connected in

- Parallel
- Series
- Earthed
- None of the above

Q.2 Primary winding of a transformer _____

- Is always a high voltage winding
- Is always a low voltage winding
- Could either be a low voltage or high voltage winding
- Cannot be determined

Q.3 Lenz law shows

- Magnitude of the current
- Magnitude of the current
- Direction of the current
- Power factor

Q.4 Capacitor is used in

- AC circuits
- DC circuits
- Both
- Cannot say

Q.5 Which winding has more number of turns?

- Low voltage winding
- High voltage winding

- c) Primary winding
- d) Secondary winding
- Q.6 What is the number of positive plates in a battery cell?
 - a) One more than the negative plates
 - b) Two less than the negative plates
 - c) One less than the negative plates
 - d) Two more than the negative plates
- Q.7 What is the phase difference between voltage and current?
 - a) 90 degree b) 60 degree
 - c) 120 degree d) Zero
- Q.8 In a star connected system, the current flowing through the line is
 - a) Greater than the phase current
 - b) Equal to the phase current
 - c) Lesser than the phase current
 - d) None of these
- Q.9 A $68\ \Omega$ resistor is connected across the terminal of a 3 V battery. The power dissipation of the resistor is
 - a) 132 mW b) 13.2mW
 - c) 22.6 mW d) 226 mW
- Q.10 How much continuous current can be drawn from a 60 Ah battery for 14 h?
 - a) 42.8 A b) 428 A
 - c) 4.28 A d) 4.2 A

SECTION-B

- Note:** Objective type questions. All questions are compulsory. (10x1=10)
- Q.11 Which is the instrument used for measuring Voltage?
 - Q.12 What is Advantage of AC use?
 - Q.13 What is power factor?

- Q.14 When earthing is done?
- Q.15 What are the characteristic of stepper motors?
- Q.16 What is the use of ELCB?
- Q.17 What type of motors are used to drive pumps?
- Q.18 What is a proof motor?
- Q.19 What do you mean by light fan circuit?
- Q.20 What is the use of isolation transformer?

SECTION-C

- Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)
- Q.21 Where are maintenance free batteries used?
 - Q.22 What is the difference between a neural and earth wire?
 - Q.23 What are the applications of stepper motors?
 - Q.24 What are the various parameters of AC power?
 - Q.25 How voltage is measured?
 - Q.26 What is EMF and how it is different from Voltage?
 - Q.27 Derive the EMF equation of a transformer.
 - Q.28 What are the various applications of electric power?
 - Q.29 Write the relation between the line and phase value of voltage and current in a balanced star connected load?
 - Q.30 What are various types of fuses?
 - Q.31 A 400 V is applied to three star connected identical impedances each consisting of a $30\ \Omega$ resistance in series with $3\ \Omega$ inductance reactance. Find line current.
 - Q.32 What is maintenance free battery?
 - Q.33 What are the various types of earthing?
 - Q.34 What is servo motor?
 - Q.35 Write in brief about Semi-Conductors?