

No. of Printed Pages : 4  
Roll No. ....

220921

**2nd Sem / Electrical**  
**Subject : Electrical Networks**

Time : 3 Hrs.

M.M. : 60

**SECTION-A**

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 The amplitude of sinusoidal current is \_\_\_\_\_ (CO2)
- a) 1.11                      b) 1.57  
c) 1.414                    d) 0.637
- Q.2 The unit of reactive power is \_\_\_\_\_. (CO2)
- a) Volts  
b) Volt-ampere  
c) Watts  
d) Volt-ampere reactive
- Q.3 If the frequency of power supply is 60 Hz, the time period of one cycle will be (CO2)
- a) 0.02 seconds            b) 20 milli-seconds  
c) 16.67 milli-seconds    d) 0.1667 seconds

(1)

220921

- Q.4 The maximum value of sine wave AC voltage is 10 V, the r.m.s value of this will be (CO3)
- a) 1.414 V                      b) 14.14 V  
c) 6.060 V                      d) 7.070 V
- Q.5 In a pure inductive a.c circuit \_\_\_\_\_. (CO3)
- a) Voltage leads the current by  $90^\circ$   
b) Current leads the voltage by  $90^\circ$   
c) Voltage lags the current by  $90^\circ$   
d) Current is in phase with voltage
- Q.6 The power factor at resonance in R.L.C Series circuit is \_\_\_\_\_. (CO3)
- a) 0                                      b) Unity  
c) 0.5 lagging                      d) 0.5 leading

**SECTION-B**

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 An electrical network with 6 independent nodes will have \_\_\_\_\_ Loop Equations. (CO1)
- Q.8 When a source is delivering maximum power to the Load, the efficiency will be (CO1)
- Q.9 An inductive coil has negligible resistance and inductance of 0.1 Henry is connected across 220 Volt, 100 Hz Supply. The power will be \_\_\_\_\_. (CO3)

(2)

220921

- Q.10 Three linear elements of D.C. Circuit are \_\_\_\_\_ (CO1)
- Q.11 Norton's theorem is the \_\_\_\_\_ of Thevenin's theorem. (CO1)
- Q.12 It is not possible to multiply a vector quantity with a number. (T/F) (CO2)

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 What factors are responsible for induced emf. (CO2)
- Q.14 Explain Norton's theorem with an example. (CO1)
- Q.15 Define power factor in a.c circuits? State disadvantages of Low power factor. (CO2)
- Q.16 Explain with mathematical expression that power consumed in a pure capacitor is zero (CO3)
- Q.17 Describe characteristics of a RLC series circuit at resonance. (CO3)
- Q.18 Explain the use of Capacitor for Power factor improvement. (CO2)
- Q.19 Describe the phenomenon of resonance in a parallel a.c. circuit. (CO3)
- Q.20 What is the relation between True power, Apparent power and Reactive Power? Draw Power Triangle also. (CO3)

(3)

220921

- Q.21 What is three Phase system? How we can generate Three Phase supply. (CO4)
- Q.22 Mention the advantages of Three Phase system over single Phase System? (CO4)

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain the relation between Phase Voltage and Line Voltage in Star Connection with suitable diagram. . (CO4)
- Q.24 Define the following : (CO2)
- i) Average Value
  - ii) RMS Value
  - iii) Form Factor
  - iv) Peak factor
- Q.25 Describe the Mesh Analysis method to solve a D.C Network with suitable example. (CO1)

(5320)

(4)

220921