

No. of Printed Pages : 4

Roll No.

180945/170945

4th Sem / Branch : Electrical Engg

Subject:- Digital Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 $(13)_{10} = (\dots)_{2}$
a) 1101 b) 1110
c) 1100 d) 1111
- Q.2 According to associative law of multiplication
a) $A(BC) = (AB)C$ b) $C = CC$
c) $A+B = B+A$ d) None of these
- Q.3 On a K-map, grouping of 0's produces
a) SOP expression b) POS expression
c) AND-OR logic d) None of these
- Q.4Flip Flop does not have Race Around Condition
a) Master Slave b) J-K Flip Flop
c) RS Flip-Flop d) D Flip-Flop
- Q.5 When the applied input to a NOT gate is high, the output is
a) High or 1 b) Low or 0
c) High or 0 d) Low or 1
- Q.6 Distinct digits used in Decimal Number system are
a) 0 to 7 b) 0 to 8
c) 0 to 9 d) 0 to 10

(1)

180945/170945

Q.7 AD-multiplexer can be used as

- a) Encoder b) Decoder
c) LCD Device d) None of these

Q.8 The most suitable gate used in the comparator circuit is

- a) AND b) OR
c) XOR d) NOT

Q.9 How many bytes are there in the Binary Number 1110000111001100

- a) 3 b) 2
c) 4 d) 8

Q.10 A 1:32 Demux has.....output data lines

- a) 32 b) 1
c) 16 d) None of these

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define term Latch
- Q.12 What is Universal Shift Register?
- Q.13 Write any two names of D/A convertor.
- Q.14 Name different types of Sequential Circuits.
- Q.15 Define Monotonicity
- Q.16 $(101110110)_2 = (\dots)_8$
- Q.17 Draw the symbol of EX-NOR gate
- Q.18 What is Hexadecimal Number System?
- Q.19 Define Analog to Digital Convertor
- Q.20 Write any two application of Counter.

(2)

180945/170945

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What do you mean by Number System? How many number system are used in Digital electronics? Explain in detail.
- Q.22 Add the following Binary Numbers:
1) 1101010+0110110 2) 101011+110010
- Q.23 What is Logic Gate? Draw the symbol, Truth Table, Logical Expression of different types of logic gates.
- Q.24 Do the subtraction by using 2's complement method of subtraction.
1) 1101-1001 2) 10011-11001
- Q.25 Explain Block diagram, Logical expression Truth Table of Octal to Binary Encoder.
- Q.26 Design Block diagram, Truth Table, Logical expression of BCD to 7 segment Decoder
- Q.27 Differentiate between MUX and DEMUX
- Q.28 Draw the symbol, logical expression, truth table and pulse operation of EX-OR gate
- Q.29 Solve the following Boolean expression
1) $ABCD + ABC\bar{D} + AB\bar{C} + A\bar{B}$
2) $XYZ [XY + \bar{Z} (YZ + XZ)]$
- Q.30 State and explain Demorgan's Theorems.
- Q.31 Describe Ring Counter in detail with Truth Table and Logical circuit.
- Q.32 Explain the working of SIPO shift register with the help of pulse diagram.

(3)

180945/170945

- Q.33 Discuss truth table, logic diagram and logical expression of a Half Adder.
- Q.34 What is DEMUX? Design a 1:8 DEMUX by using truth table logical expression and logical circuit.
- Q.35 What is the difference between Digital Signal and Analog Signal?

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Minimize the following Boolean expression using K-Map and realize the logic Circuit using NAND gates only.
 $F(A,B,C,D) = \sum (0,1,2,5,7,13,14) + d(3,6,9)$
- Q.37 Explain the Logic Diagram, Truth Table and Operation of Master-Slave J-K flip Flop and show how it will overcome Race Around Condition of the flip-flop
- Q.38 Write short note on following:
a. R/2R Ladder Digital to Analog Converter
b. Dual Slope Analog to Digital Converter

(4800)

(4)

180945/170945