

No. of Printed Pages : 4 180832/170832/120832
Roll No. /030832/031034/106544

3rd Sem
Subject:- Digital Eltx - I

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 One byte is equal to _____ nibble. (CO2)
a) 1 b) 2
c) 3 d) 4
- Q.2 The binary number of decimal numbers 32 is _____. (CO2)
a) (100000)₂ b) (101100)₂
c) (111111)₂ d) (010101)₂
- Q.3 What are the advantages of the digital systems? (CO4)
a) High-efficiency b) Uses less bandwidth
c) Encryption d) All of the above
- Q.4 According to Boolean algebra, which of the following is Valid? (CO5)
a) $X+X=1$ b) $1.X=1$
c) $0.X=X$ d) $X.X=1$
- Q.5 A half adder consists _____. (CO6)
a) one input one output b) one input two outputs
c) two inputs two outputs d) two inputs one output

- Q.6 The output of multiplexer depends on its _____. (CO7)
a) Data outputs b) Data inputs
c) Selected inputs d) None of the above

- Q.7 The group of flip-flops is also known as _____. (CO8)
a) Registers b) Counters
c) Encoders d) None of the above

- Q.8 How much data the shift register can store? (CO10)

- a) only one bit b) only two bits
c) only three bits d) None of the above

- Q.9 A four variable K-Map has _____ cells. (CO5)

- a) 4 b) 16
c) 8 d) 10

- Q.10 The base of radix represents _____. (CO10)

- a) Number of bits b) Number of digits
c) Number of symbols d) All of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 _____ signal is used in communication process to minimize the effect of noise. (CO1)
- Q.12 Which logic unit is the fastest of all the logic families? (CO2)
- Q.13 Half adder has _____ number of inputs. (CO5)
- Q.14 Name the Boolean Law: (Co6)
 $A+B=B+A$
- Q.15 PIPO stands for _____. (Co10)

(1) 180832/170832/120832
/030832/031034/106544

(2) 180832/170832/120832
/030832/031034/106544

- Q.16 A device which converts a decimal number into BCD form is called _____. (CO8)
- Q.17 How many NOR gates are required to obtain AND operation? (CO12)
- Q.18 How many select lines will a 16 to 1 multiplexer will have. (CO7)
- Q.19 How many flip flops are required to construct a decade counter. (CO8)
- Q.20 The process of entering data into a ROM is called _____. (CO12)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 i) Define digital signal. (CO1)
ii) Convert $(101011)_2$ into Gray Code (CO3)
- Q.22 Perform (Co3)
I) $(16)_{10} - (5)_{10}$ using 1's complement.
ii) $(32.7)_8$ to Binary .
- Q.23 Explain NOR gate with its truth table and circuit diagram. (CO4)
- Q.24 Simplify the expression $(A+C)(AD+AD^{---}) + AC + C$ using Boolean algebra. (CO5)
- Q.25 Write short note on four-bit adder. (CO6)
- Q.26 Give the basic function of MUX. Draw block diagram and Truth Table of 8x1 MUX. (CO7)
- Q.27 Differentiate between synchronous and asynchronous counter. (CO9)

- Q.28 What is race around condition? and how it can be removed? (CO8)
- Q.29 Write short notes on postulates of Boolean algebra. (CO5)
- Q.30 Explain the working of 3-to-8 decoder with truth table? (CO7)
- Q.31 Explain the operation of D flip-flop with diagram. (CO7)
- Q.32 Explain NOR gate with truth table. (CO4)
- Q.33 Explain with diagram about SISO shift register. (CO10)
- Q.34 What do you mean by counter? Explain applications of counters. (CO9)
- Q.35 Explain successive approximation A/D converter. (CO11)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Draw a k-map to reduce the function and realize the reduced function by using NAND gates. (CO3)
 $F = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$.
- Q.37 What is an encoder? Draw the logic circuit of a decimal to BCD encoder and its working. (CO7)
- Q.38 Write short note on :
I) De Morgan's theorem (CO3)
ii) EPROM (CO12)
- (**Note:** Course outcome/CO is for office use only)