

No. of Printed Pages : 4
Roll No.

181043/171043

4th Sem / Eltx
Subject:- Power Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Number of layers in SCR is (CO1)
a) 1 b) 2
c) 3 d) 4
- Q.2 SCR behaves as _____ switch (CO1)
a) Mechanical b) Bi-directional
c) Unidirectional d) None of the above
- Q.3 Which among the following is a gate less semiconductor device (CO1)
a) IGBT b) DIAC
c) TRIAC d) JFET
- Q.4 DIAC is turned on using which technique? (CO2)
a) Gate voltage triggering
b) Gate current triggering
c) Breakover voltage triggering
d) Breakover current triggering
- Q.5 FWD is used in _____ load (CO4)
a) Resistive b) Inductive
c) Capacitive d) None of the above

(1)

181043/171043

- Q.6 A cycloconverter is a (CO7)
a) AC to DC converter b) DC to AC converter
c) AC to AC converter d) DC to DC converter
- Q.7 Class-A choppers operates in _____ quadrant (CO7)
a) 1st b) 2nd
c) 3rd d) 4th
- Q.8 AUPS with 150 AH, 12 V battery is connected to a 300W load. What will be backup time of the UPS (CO7)
a) 3 hour b) 6 hour
c) 9 hour d) 12 hour
- Q.9 Snubber circuit is used for (CO2)
a) Triggering a SCR
b) Prevent accidental triggering of SCR
c) Commutation of SCR
d) Prevent accidental commutation of SCR
- Q.10 _____ commutation used for AC drives (CO8)
a) Class A b) Class C
c) Class D d) Class F

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define valley point. (CO3)
- Q.12 SCR is made of germanium. (True/False) (CO1)
- Q.13 Expand FWD (CO4)
- Q.14 Define PIV (CO2)
- Q.15 TRIAC is a bidirectional device. (True/False) (CO1)

(2)

181043/171043

- Q.16 The primary source of power in ON-line UPS is battery. (True/False) (CO6)
- Q.17 Series inverter uses _____ type of commutation. (CO7)
- Q.18 The value of latching current is less than that of holding current. (True/False) (CO2)
- Q.19 Average output voltage of a single phase full wave fully controlled rectifier is less than that of single phase full wave fully controlled rectifier (True/False) (CO4)
- Q.20 Dual converter circuit are designed only for single phase system. (True/False) (CO7)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain any two triggering techniques of SCR (CO)
- Q.22 Explain the need of heat sinks for power electronic devices (CO1)
- Q.23 Draw and explain the vi characteristics of DIAC (CO2)
- Q.24 Explain any two commutation techniques. (CO2)
- Q.25 Explain the working of UJT as a relaxation oscillator (CO3)
- Q.26 Differentiate between series and parallel inverter (CO7)

- Q.27 What is the difference between controlled and uncontrolled rectifier. (CO5)
- Q.28 Explain the working of Class A chopper (CO7)
- Q.29 Explain the working of a cycloconverter (CO7)
- Q.30 Explain regenerative braking (CO7)
- Q.31 Compare AC and DC drives (CO8)
- Q.32 Explain the construction of TRIAC (CO1)
- Q.33 Explain the working of Offline UPS (CO6)
- Q.34 Explain the parallel connection of SCR (CO2)
- Q.35 Explain the slip power control method of AC drives. (CO2)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 With a neat sketch explain the VI characteristics of a SCR (CO2)
- Q.37 Explain the working of a single phase full wave fully controlled rectifier with inductive load. Also draw the waveform for input and output voltages for the same. (CO4)
- Q.38 With a neat sketch explain the speed control of DC motor using a controlled rectifier (CO8)
- (**Note:** Course outcome/CO is for office use only)