

No. of Printed Pages : 4
Roll No.

180933/170933

Electrical Engg.
Subject:- Electronics II

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Heat sink reduces _____
a) transistor power b) ambient temperature
c) junction temperature d) collector current
- Q.2 Complementary push pull amplifier use _____
a) two PNP transistors
b) two NPN transistors
c) one NPN and other PNP
d) None of the above
- Q.3 In series RLC circuit, below resonant frequency, impedance is _____
a) capacitive b) inductive
c) resistive d) None of the above
- Q.4 The effects of negative feedback are following except _____
a) Reduction in gain
b) reduction in output impedance
c) Increase in distortion

(1)

180933/170933

- d) increase in bandwidth
- Q.5 The material with the piezo-electric effect is
a) Quartz b) Rochelle salt
c) Tourmaline d) All of the above
- Q.6 In series RC circuit, voltage across the resistance
a) is in phase with current
b) is in phase with source voltage
c) lead source voltage by 90°
d) lag the current by 90°
- Q.7 A diode clipper circuit
a) inserts dc level
b) produces average of input
c) removes part of waveform
d) increases peak value
- Q.8 The multivibrator which does not require any trigger is _____
a) Astable multivibrator
b) Monostable multivibrator
c) Bistable multivibrator
d) None of the above
- Q.9 The output of IC 7915 is _____
a) +15V b) -15V
c) +5V d) -5V
- Q.10 Operational amplifier amplify _____
a) ac only b) dc only
c) ac and dc both d) None of the above

(2)

180933/170933

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What is collector efficiency?
- Q.12 What is feedback in amplifier?
- Q.13 What is the efficiency of class C power amplifier?
- Q.14 Which feedback is used in oscillator?
- Q.15 In which region transistor act as a amplifier?
- Q.16 Define the term non-linear wave shaping circuit.
- Q.17 Define switches. What are different types of switches?
- Q.18 What is the output waveform of multivibrator?
- Q.19 Which pin in IC 555 is used for threshold voltage?
- Q.20 What is adjustable voltage regulator?

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Distinguish between voltage and power amplifier.
- Q.22 Define the terms:- power dissipation capability, distortion.
- Q.23 What is the effect of negative feedback on input resistance?
- Q.24 Why heat sink is important while using power amplifier?
- Q.25 Compare series and parallel resonance circuit.
- Q.26 Discuss the features of emitter follower circuit.
- Q.27 Explain different types of feedback used in amplifiers.

(3) 180933/170933

- Q.28 How an op-amp is used as integrator circuit?
- Q.29 Explain the working of Colpitt oscillator.
- Q.30 Discuss the operation of CVTs.
- Q.31 How a 555 timer is used as monostable multivibrator?
- Q.32 What are the advantages of double tuned amplifier over single tuned amplifier?
- Q.33 Discuss the applications of operational amplifier.
- Q.34 How diode is used as wave shaping circuit? Explain with neat sketches.
- Q.35 Discuss the working principle of SMPS.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Discuss with the help of circuit diagram, the push pull amplifier. Describe advantages and disadvantages of push pull amplifier.
- Q.37 Explain the working and construction of Wein Bridge Oscillator.
- Q.38 Write a short note on any two:-
 - a) Piezoelectric crystal
 - b) Barkhausen criteria for oscillations
 - c) Hartley oscillator

(5480) (4) 180933/170933