

- Q.34 What is thermal drift?  
Q.35 Explain active filter and classify them.

### SECTION-D

**Note:** Long Answer type question. Attempt any two questions out of three questions. (2x10=20)

- Q.36 How the IC 555 work as as astable multivibrator explain with neat diagram?  
Q.37 Draw and explain ADC comparator?  
Q.38 Write a Note on :  
a) OP-AMP as differentiator  
b) Schmitt trigger

No. of Printed Pages : 4  
Roll No.....

123644/073644

### 4th Sem / Electronics & Instrumentation Subject : Linear & Digital Integrated Circuits

**Time : 3 Hrs.**

**M.M. : 100**

### SECTION-A

**Note:** Multiple choice questions. All questions are compulsory. (10x1=10)

- Q.1 An ideal OP-AMP have  
a) Infinite input impedance  
b) Zero output impedance  
c) Infinite bandwidth  
d) All of above
- Q.2 A voltage follower \_\_\_\_\_  
a) Has a voltage of 1  
b) Is non inverting  
c) Has no feedback resistor  
d) All of above
- Q.3 NAND gate is \_\_\_\_\_  
a) AND gate followed by NOT gate  
b) OR gate followed by NOT gate  
c) NOT gate followed by AND gate  
d) NOT gate followed by OR gate
- Q.4 In a multiplexer, if there are 4 input lines and 1 output line, then number of select lines will be  
a) 3  
b) 0  
c) 2  
d) 1

- Q.5 IC 741 has \_\_\_\_\_ number of pins.  
 a) 4                                      b) 16  
 c) 8                                        d) 20
- Q.6 An instrumentation amplifier is high  
 a) Output impedance    b) Power gain  
 c) CMRR                      d) supply voltage
- Q.7 The Common mode gain is  
 a) Very high                      b) Very low  
 c) Always unity                  d) Unpredictable
- Q.8 In a J-K flip flop, when J=1 and K=1 then it will be consider as  
 a) Set condition                  b) reset condition  
 c) No change                      d) Toggle condition
- Q.9 What is a filter  
 a) Frequency damping circuit  
 b) Frequency selective circuit  
 c) Amplitude selective circuit  
 d) Amplitude damping circuit
- Q.10 The input to OP-AMP open loop comparator is sinusoidal signal, the output of comparator is  
 a) Square wave                  b) sine wave  
 c) Cosine wave                  d) Triangular wave

### SECTION-B

**Note :** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Expand DAC.  
 Q.12 Define slew rate.

- Q.13 Define Encoder.  
 Q.14 Expand CMRR.  
 Q.15 Define open loop gain.  
 Q.16 IC 555 has \_\_\_\_\_ no. of pins.  
 Q.17 Define Thermal drift.  
 Q.18 Draw symbol of NOR gate.  
 Q.19 Define Active filter.  
 Q.20 The unwanted signal is called \_\_\_\_\_.

### SECTION-C

**Note :** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain difference between digital and linear ICs.  
 Q.22 Explain what factors affect the input offset voltage.  
 Q.23 What is Demultiplexer? Explain.  
 Q.24 Write the characteristic of an ideal OP-AMP.  
 Q.25 Draw pin diagram of IC 555.  
 Q.26 Explain different feedback configurations.  
 Q.27 Define SVRR and Slew rate of OP-AMP.  
 Q.28 Describe working of phase lock loop.  
 Q.29 Explain block diagram of active low pass filter.  
 Q.30 Draw a basic comparator circuit.  
 Q.31 How OP-AMP can be used as inverting amplifier? Explain.  
 Q.32 Draw common mode configuration of OP-AMP.  
 Q.33 Explain working of Encoder.