

No. of Printed Pages : 4 181031/171031/121031
Roll No. /031031

**3rd Sem / Eltx., Mecatronics, Med. Eltx, Power Eltx,
Elect, & Eltx. Engg.**

Subject:- Electronic Devices and Circuits / Analog Eltx - II

Time : 3Hrs. M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 In multistage amplifier, capacitor is used
a) to match impedance
b) to couple 2 stages
c) to limit the bandwidth
d) to limit the current
- Q.2 Which of the following is expensive
a) Direct Coupling
b) R-C Coupling
c) Transformer coupling
d) All of the above
- Q.3 Which of the following is common collector amplifier
a) Push Pull amplifier
b) Emitter follower
c) Differential amplifier
d) None of these
- Q.4 Heat sink is mostly used in
a) Audio amplifier

- b) Small signal amplifier
c) Large signal amplifier
d) All of the above

- Q.5 When negative voltage feedback is applied to an amplifier its bandwidth
a) increased b) decreased
c) remain same d) None of the above
- Q.6 RC network in phase shift oscillator produces a phase shift of
a) 180° b) 360°
c) 90° d) 0°
- Q.7 When resonance occur in series or parallel resonant circuit the circuit behaves as
a) inductive b) capacitive
c) Resistive d) None
- Q.8 As astable multivibrator has _____ stable.
a) one b) two
c) three d) No
- Q.9 An ideal op-amp has
a) infinite voltage gain
b) infinite input resistance
c) zero output resistance
d) All of the above
- Q.10 The output voltage of IC 7909 is
a) +9 v b) -9 v
c) +12 v d) -5 v

(1) 181031/171031/121031
/031031

(2) 181031/171031/121031
/031031

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Transformer is not used in regulated power supply.
- Q.12 The gain and input resistance of an ideal op-amp are _____.
- Q.13 Full form of PSRR is _____.
- Q.14 As oscillator employs _____ feedback.
- Q.15 What is piezoelectric effect?
- Q.16 Feedback network consists of resistance, capacitance and inductances. (True/False)
- Q.17 Negative feedback is employed in oscillators.
- Q.18 Define gain in amplifier.
- Q.19 What is the significance of coupling capacitor?
- Q.20 Give working principle of crystal oscillator?

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain Direct coupled amplifier.
- Q.22 Explain Class AB amplifier.
- Q.23 Describe frequency response and Bandwidth.
- Q.24 Describe single ended power amplifier.
- Q.25 What do you understand by heat dissipation curve explain.

- Q.26 Derive expression for gain of an amplifier employing negative feedback.
- Q.27 Explain the working of emitter follower circuit.
- Q.28 Explain Wein Bridge Oscillator with circuit diagram.
- Q.29 Define CMRR and PSRR.
- Q.30 Explain op-amp as an adder.
- Q.31 Describe block diagram of regulated DC power supply.
- Q.32 Explain Bistable multivibrator with circuit diagram.
- Q.33 Explain IC 555 working with Pin diagram.
- Q.34 Differentiate between voltage and Power amplifier.
- Q.35 How feedback affects the distortion in amplifier.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain the working of IC 723 variable voltage regulator with diagram.
- Q.37 Describe push pull amplifier with circuit diagram in detail.
- Q.38 Define Barkhausen criterion and explain the working of phase shift oscillator.