

No. of Printed Pages : 4  
Roll No. ....

181035

**3rd Sem / Eltx**

**Subject:- Network Filters and Transmission Lines**

Time : 3Hrs.

M.M. : 100

**SECTION-A**

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 How many terminals a two port network has  
a) 1                                      b) 2  
c) 3                                      d) 4
- Q.2 A two port is reciprocal or bilateral provided  
a)  $Z_{11} = Z_{22}$                                       b)  $Z_{11} = Z_{12}$   
c)  $Z_{12} = Z_{21}$                                       d)  $Z_{21} = Z_{22}$
- Q.3 Characteristic impedance for asymmetrical network at both the ports is  
a) Same                                      b) Different  
c) Defined                                      d) Not defined
- Q.4 in symmetrical T network what is the values of series arm impedance  
a)  $Z_1$                                       b)  $Z_1/2$   
c)  $Z_2$                                       d)  $Z_2/2$
- Q.5 For a prototype LPF, the phase constant  $\beta$  in the attenuation band is given by \_\_\_\_\_  
a)  $\pi$                                       b) 0  
c)  $\pi/2$                                       d)  $\pi/4$

(1)

181035

- Q.6 A band pass filter may be obtained using a high pass filter followed by  
a) Low Pass Filter                                      b) High Pass Filter  
c) Band Pass Filter                                      d) Band Reject Filter
- Q.7 For a Prototype LPF, series arm component is  
a) Capacitance                                      b) Inductance  
c) Resistance                                      d) None of the above
- Q.8 Input impedance of short circuited loss line with length  $l/4$  is  
a) Infinity  
b) Zero  
c) Characteristic impedance  
d) None of the above
- Q.9 An active network has  
a) an emf source                                      b) a current source  
c) Both                                      d) None of the above
- Q.10 If  $K=0$ , Then VSWR will be \_\_\_\_\_  
a) 0                                      b) 1  
c) 2                                      d) All of the above

**SECTION-B**

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 A two port network has \_\_\_\_\_ terminal. (Two/four)
- Q.12 In an a symmetrical T-network, series arm in both sides have same impedance. (True/False)
- Q.13 Define attenuators.

(2)

181035

- Q.14 Decibel is a unit of \_\_\_\_\_ (Capacitance / attenuation)
- Q.15 Inductor is an \_\_\_\_\_ element. (active/passive)
- Q.16 Name primary constant of transmission line.
- Q.17 Expand VSWR.
- Q.18 Write full form of LPF.
- Q.19 R,L,C and G are known as secondary constant of transmission line. (True/False)
- Q.20  $Z_{oc} * Z_{sc} =$  \_\_\_\_\_

### SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Drive an expression for characteristic impedance of 'T' network.
- Q.22 What is asymmetrical network? Explain iterative impedance of an asymmetrical network.
- Q.23 Differentiate between Linear and non-linear network.
- Q.24 Explain concept and significance of Iterative Impedance.
- Q.25 Design a symmetrical 'T' attenuator?
- Q.26 What are the uses of attenuator?
- Q.27 Draw and Drive the design equation of L-type attenuator.
- Q.28 Draw and Explain the characteristics (Phase shift v/s frequency) of T filter.
- Q.29 Explain concept of band pass filter

- Q.30 What is difference between active and passive filter? Explain in detail.
- Q.31 What is a Stub? Explain the principal of impedance matching using stub.
- Q.32 A lossless line is terminated in pure resistance of 600W if characteristic impedance is 400W. Find value of SWR.
- Q.33 Explain the concept of transmission line at high frequency.
- Q.34 Write a short note on crystal filter.
- Q.35 List different type of Transmission line.

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 What is a symmetrical network? Explain concept of propagation constant and attenuation constant in a symmetrical 'T' network.
- Q.37 Write a short note on  
a) Band Pass Filter  
b) SWR and VSWR
- Q.38 What are the various type of distortion in transmission line and also explain the condition for minimum distortion?