

- Q.24 Discuss the effective of negative feedback on gain, distortion and bandwidth.
- Q.25 Explain Emitter follower circuit
- Q.26 What are the advantages of tuned amplifiers?
- Q.27 Write short note on single tuned voltage amplifiers.
- Q.28 Draw pin diagram of 555 timer?
- Q.29 Explain diode clipping circuits in brief
- Q.30 Explain working of bistable multivibrator?
- Q.31 Explain SMPS.
- Q.32 Explain RC as integrator circuits.
- Q.33 Explain UPS
- Q.34 What is an oscillator. Write Barkhausen criteria.
- Q.35 Explain operation of Wien bridge oscillator.

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 Explain working of complementary symmetry push pull amplifier.
- Q.37 Explain working of RC phase oscillator.
- Q.38 Explain working and applications of transistor inverter circuit using power transistors.

No. of Printed Pages : 4

Roll No.

127543

4th Sem / Branch : Fine Tech & Safety
Subject:- Electronic Devices and Circuits

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 In class B amplifier operating point is located at ____
 a) Centre of load line b) Near saturation
 c) Cut off point d) None
- Q.2 Distortion is minimum in ____ type of amplifiers
 a) Class A b) Class C
 c) Class AB d) Push Pull
- Q.3 In class A amplifier, collector current flows for ____
 a) Less than half cycle b) Half the cycle
 c) Entire cycle d) Less than entire cycle
- Q.4 The Hartley Oscillator uses
 a) Negative feedback b) Negative
 c) Sinusoidal d) None
- Q.5 Transistor can be used as ____ for application

- a) Switch b) Amplifier
c) Inverter d) All
- Q.6 _____multivibrators are used as flip-flop in digital circuits
- a) Astable b) Monostable
c) Bistable d) None
- Q.7 An oscillator always needs an amplifier with_____:
- a) Negative feedback
b) Positive feedback
c) Both types of feedback
d) LC tank circuit
- Q.8 The impedance of RLC series circuit at resonance____
- a) Resistive b) Capacitive
c) Inductive d) None
- Q.9 Constant dc output voltage is obtained in_____power supply:
- a) Regulated b) Non regulated
c) Negative d) None
- Q.10 A clamper circuit is known as_____
- a) Average circuit b) DC resistor
c) AC resistor d) Inverter

(2)

127543

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Output wave form of 555 timer is_____?
- Q.12 What is tuned amplifier?
- Q.13 _____multivibrator is called one shot multivibrator?
- Q.14 In integrator circuit, output is taken across_____
- Q.15 What is negative feedback?
- Q.16 What is voltage amplifier?
- Q.17 Class_____has highest collector efficiency
- Q.18 The negative feedback increases_____in amplifier.
- Q.19 Push pull amplifier uses class_____?
- Q.20 The distortion is minimum in_____type of power amplifiers.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain the term collector Efficiency and Distortion in Amplifiers.
- Q.22 Explain positive feedback and its importance
- Q.23 Explain in brief operation of class A amplifier.

(3)

127543