

No. of Printed Pages : 4
Roll No.

181035

4th Sem / Branch : Eltx. Engg.
Subject:- Network Filters & Transmission Lines

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Which of the following is not a non-linear element?
a) Diode b) Transistor
c) FET d) Inductor
- Q.2 A network having a battery source in one of its arms is called.....
a) Passive network b) Recurrent network
c) Active network d) Unilateral network
- Q.3 Propagation constant parameter is used in.....
a) Inverse network
b) Bilateral network
c) Asymmetrical network
d) Symmetrical network
- Q.4 A variable attenuator which needs to vary only two element is.....
a) T type attenuator
b) π type attenuator
c) Bridge T type attenuator

(1)

181035

- d) Lattice attenuator
- Q.5 Neper is equal to.....
a) 115.1 x attenuation in dB
b) 11.51 x attenuation in dB
c) 1.151 x attenuation in dB
d) 0.1151 x attenuation in dB
- Q.6 In order to balance π type attenuator, the arm which is splitted in two halves is.....
a) shunt arm
b) series arm
c) bridge arm
d) both series and shunt arm
- Q.7 The pass band of LPF is
a) above f_c
b) below f_c
c) from dc to f_{c1} and above f_{c2}
d) from f_{c1} to f_{c2}
- Q.8 A filter having cut-off frequency, $f_c = 1/4\pi\sqrt{LC}$ is
a) Prototype BPF b) Prototype LPF
c) Prototype BSF d) Prototype HPF
- Q.9 In a lossless line; characteristics impedance is given by.....
a) Z_0 b) Z_{oc}
c) Z_{sc} d) $Z_{oc} \cdot Z_{sc}$

(2)

181035

- Q.10 Loading is a process in transmission line to.....
- Decrease inductance of line
 - Artificially boost inductance of line
 - Increasing resistance of line
 - Increasing shunt capacitance of line

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What is a port?
- Q.12 What is an active network
- Q.13 What do you mean by insertion loss?
- Q.14 Draw an unbalanced π -type attenuator?
- Q.15 Whether a lattice attenuator is a balanced network?
- Q.16 What is the value of attenuation in any symmetrical attenuator?
- Q.17 Draw the diagram of prototype of low pass T filter.
- Q.18 What is the formula for cut-off frequency of HPF?
- Q.19 What is the unit of attenuation constant (α)
- Q.20 Define the term reflection coefficient.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What are active and passive filters?
- Q.22 How can you distinguish between symmetrical and asymmetrical networks?
- Q.23 What do you mean by transmission lines? What are its various types?

(3)

181035

- Q.24 Design a prototype section of band pass filter.
- Q.25 Explain the significance of characteristics impedance.
- Q.26 What is an attenuator? Name its various types.
- Q.27 Write a short note on propagation constant of a transmission line.
- Q.28 Deduce the relationship between decibel and Neper.
- Q.29 What is an image impedance?
- Q.30 Define Z and Y parameters of a two port networks?
- Q.31 What is a STUB? What is the purpose of stub in a transmission lines?
- Q.32 Derive an expression for relationship between VSWR and reflection coefficient K.
- Q.33 Write a short note on m-derived filter.
- Q.34 Explain lattice type of network.
- Q.35 What do you mean by loading? How is it done?

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Establish a relationship between the characteristics impedance of symmetrical π and T networks.
- Q.37 Draw the Butterworth's first order low pass filter and derive equations for it.
- Q.38 Write a short note on any two of the following:
- Ladder attenuators
 - Half section
 - Phase delay constant

(2580)

(4)

181035