

No. of Printed Pages : 4
Roll No.

220832/212832

3rd Sem /
Branch : Computer, ECE, Automation & Robotics
Sub.: Digital Electronics

Time : 3Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 Which digital gate performs the multiplication operation? (CO2)
a) AND gate b) OR gate
c) NOR gate d) NAND gate
- Q.2 A decade counter counts _____ number of clocks. (CO3)
a) 4 b) 8
c) 10 d) 16
- Q.3 One byte is equals to _____ bits. (CO1)
a) 6 b) 8
c) 5 d) 7
- Q.4 A four variable K-Map has _____ cells. (CO2)
a) 4 b) 16
c) 8 d) 10

(1)

220832/212832

- Q.5 The base of radix represents _____. (CO1)
a) No. of bits b) No. of digits
c) No. Of symbols d) All of above
- Q.6 The universal gate is _____. (CO2)
a) NAND gate b) OR gate
c) AND gate d) None of above

SECTION-B

Note: Objective/Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 How many NOR gates are required to obtain AND operation? (CO2)
- Q.8 PROM stands for _____. (CO5)
- Q.9 In Boolean Algebra, $(A \cdot \bar{A}) + A = ?$ (CO2)
- Q.10 2's complement of 100101 is _____. (CO1)
- Q.11 A flip flop has _____ stable states. (CO4)
- Q.12 Gray code equivalent to binary code 1011 is _____. (Co1)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Differentiate between weighted and non - weighted codes. (CO1)

(2)

220832/212832

- Q.14 Convert $(67)_{10} = (?)_2 = (?)_8 = (?)_{16}$. (CO1)
- Q.15 Explain AND, OR and NOT gate with symbol and truth table. (CO2)
- Q.16 Solve the Boolean expression $\bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C}$. (CO2)
- Q.17 Give the basic function of MUX. Draw block diagram and truth table of 8x1 MUX. (CO3)
- Q.18 Explain 4 bit full adder circuit with diagram. (CO3)
- Q.19 Explain with diagram D flip flop. (CO4)
- Q.20 Explain with diagram SISO shift register. (CO4)
- Q.21 Explain Successive Approximation ADC. (CO5)
- Q.22 Explain classification of Semiconductor Memories. (CO5)

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)
- Q.23 Simplify K-Map and realize the circuit with NAND gates only. (CO2)
- $Y = \sum m(0, 1, 3, 5, 7, 9, 11, 13, 15)$
- Q.24 Explain with diagram working of Synchronous Decade Counter. (CO4)
- Q.25 Define Encoder. Explain its function using block diagram. (CO3)