

No. of Printed Pages : 4

Roll No. ....

221014/212817

**1st / Branch ECE / Instrumentation & Control Engg/  
Automation & Robotics/ Medical Electronics**

**Subject : Fundamentals of Electrical Engg**

Time : 3 Hrs.

M.M. : 60

### SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 Unit of Resistance is (CO1)

- a) Ampere                      b) Ohm
- c) Joule                        d) Watt

Q.2 Ammeter is used for measuring (CO1)

- a) Current                      b) Voltage
- c) Resistance                d) Power

Q.3 An ideal current source has (CO2)

- a) Zero                        b) One
- c) Infinity                    d) Six

Q.4 Unit of Capacitance is (CO1)

- a) Ohm                        b) Watt
- c) Farad                      d) Coulomb

(1) 221014/212817

Q.5 Unit of Time Period is (CO3)

- a) Ohm                        b) Sec
- c) Hertz                      d) Watt

Q.6 In Lead acid cell Negative plate is made of (CO5)

- a) Lead
- b) Lead oxide
- c) Iron
- d) Lead Sulphate

### SECTION-B

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Unit of Inductance is\_\_\_\_\_ (CO1)

Q.8 Unit of Power is\_\_\_\_\_ (CO1)

Q.9 Unit of frequency is\_\_\_\_\_ (CO3)

Q.10 Unit of Impedance is\_\_\_\_\_ (CO3)

Q.11 Minimum value of Power factor is\_\_\_\_\_ (CO3)

Q.12 Unit of flux is\_\_\_\_\_ (CO4)

(2) 221014/212817

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Two Capacitors of 3 farad and 6 farad are first connected in series and then in parallel. Find the total equivalent capacitance in each case. (CO1)
- Q.14 Explain the factors on which resistance of a conductor depends (CO1)
- Q.15 Define Faraday's Laws of Electro Magnetic induction. (CO4)
- Q.16 Define and explain Ohm's Law (CO2)
- Q.17 Define Super position Theorem (CO2)
- Q.18 Explain Series and Parallel connection of Resistance. (CO1)
- Q.19 Define and explain Average value of AC (CO3)
- Q.20 Explain series resonance in R-L-C Series Circuit. (CO3)
- Q.21 Derive the expression for power Consumed in pure Inductor (CO4)
- Q.22 Explain the reactions that take place at Anode and Cathode during Discharging in Lead acid cell. (CO5)

(3) 221014/212817

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Define and explain Maximum Power Transfer Theorem and Thevenin Theorem (CO2)
- Q.24 Explain construction, working principle and applications of Lead Acid Battery (CO5)
- Q.25 Explain Voltage and Current Source, Symbol and Graphical representation and characteristics of ideal and practical sources. (CO2)

(1580) (4) 221014/212817