

- Q.32 Discuss truth table, logic diagram and logical expression of a Full Subtractor.
- Q.33 Explain the working of SIPO shift register with the help of pulse diagram.
- Q.34 What do you mean by DEMUX? Design a 1:4 DEMUX by using truth table, logical expression and logical circuit.
- Q.35 What is Error Correcting Coded? How it can be corrected by using parity?

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Minimize the following Boolean expression using K-Map and realize the logic Circuit using NAND gates only

$$Y = \sum (0, 1, 3, 5, 7, 9, 11, 13, 15)$$

- Q.37 Explain the following A to D Convertor with suitable diagram.
- Successive Approximation A/D Convertor
 - Stair Step ramp A/D Convertor
 - Dual Slope A/D Convertor
- Q.38 Write short note on following:
- Decade Counter
 - Universal Shift Register

No. of Printed Pages : 4
Roll No.

202445/122445/062445

4th Sem / Mechatronics Subject:- Digital Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 How many nibbles are there in 1110010101001100 binary number
- 3
 - 2
 - 4
 - 8
- Q.2 Which expression shows a POS expression
- $A(B+C)+D$
 - $(A+B+C)(C+D)$
 - $AB+CD+BC$
 - None of these
- Q.3 How many cells are there in a 4 variable K-map?
- 4 cells
 - 15 cells
 - 8 cells
 - 16 cells
- Q.4 A MUX means
- many into one device
 - one into many device
 - many into many device
 - None of these
- Q.5 _____ flip-flop does not have race around condition.
- Master Slave
 - D flip-flop
 - RS flip-flop
 - J-K flip flop

- Q.6 Which device has more operating speed?
 a) LED b) LCD
 c) Fluorescent tube d) None
- Q.7 A Demux performs the reverse operation of
 a) Decoder b) Encoder
 c) MUX d) Adder
- Q.8 In a Boolean algebra $A.1 =$ _____
 a) 0 b) A
 c) 1 d) None
- Q.9 The NOT gate performs a function known as
 a) Complementation b) Inversion
 c) Assertion d) Both (a) and (b)
- Q.10 The radix of a Decimal Number System is _____
 a) 8 b) 10
 c) 16 d) 9

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define Minterm.
 Q.12 What is Digital Signal?
 Q.13 Write full form of ASCII and EBCDIC.
 Q.14 Name different types of Counters.
 Q.15 Write any two applications of A/D converters.
 Q.16 What is Resolution?
 Q.17 Draw the symbol of EX-NOR gate
 Q.18 What is Decoder?
 Q.19 List any two applications of Multiplexer.
 Q.20 What is Latch?

(2) 202445/122445/062445

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What is the difference between Latch and Flip-Flop?
 Q.22 Divide the following Binary Numbers:
 i) 11011 by 101
 ii) 111100 by 100
- Q.23 What is Digital Signal? Explain advantages and application of Digital signal over Analog signal.
 Q.24 Convert the following Hexadecimal Numbers into Decimal Numbers:
 i) 7FFF ii) 9AD
 iii) A3B7
- Q.25 Explain Block diagram, Logical expression, Truth Table of BCD to Decimal Decoder.
 Q.26 Design Block diagram, Truth Table, Logical Expression of 4:1 MUX.
- Q.27 Differentiate between Synchronous Counter and Asynchronous Counter
 Q.28 Draw the symbol, logical expression, truth table and pulse operation of EX-OR gate.
 Q.29 Solve the following Boolean expression:
 i) $ABCD + ABC\bar{D} + AB\bar{C} + A\bar{B}$
 ii) $AB + A(B+C) + B(B+C)$
- Q.30 State and Explain the Laws of Boolean Algebra.
 Q.31 Explain the working of S-R Flip Flop by using truth table, logic diagram and pulse wave diagram.

(3) 202445/122445/062445