

- |      |   |       |
|------|---|-------|
| Q.27 | What is the difference between controlled and uncontrolled rectifier.     | (CO5) |
| Q.28 | Explain the working of Class B chopper.                                   | (CO7) |
| Q.29 | Explain the working of a cycloconverter.                                  | (CO7) |
| Q.30 | Explain regenerative braking.   | (CO7) |
| Q.31 | Define commutation. Differentiate between natural and forced commutation. | (CO2) |
| Q.32 | Explain briefly VFD.  | (CO8) |
| Q.33 | Explain the working of Online UPS.  | (CO6) |
| Q.34 | Explain series connection of SCR.   | (CO2) |
| Q.35 | Explain the slip power control method of AC drives.                       | (CO8) |

## SECTION-D

**Note: Long answer questions. Attempt any two question out of three Questions. (2x10=20)**

- Q.36 With a neat sketch explain the VI characteristics of TRIAC. (CO2)
- Q.37 Explain the working of a single phase full wave half controlled rectifier. (CO4)
- Q.38 Explain the chopper based speed control of DC motor. (CO8)

Note: Course Outcome (CO) mentioned in the question paper is for official purpose only.

No. of Printed Pages : 4

181043/171043

Roll No. ....

**4th Sem./ Electronics & Communication Engineering**  
**Subject : Power Electronics**

Time : 3 Hrs.

M.M. : 100

## SECTION-A

**Note: Multiple type Questions. All Questions are compulsory. (10x1=10)**

- Q.1 Number of PN junction of SCR is (CO1)  
a) 1 b) 2  
c) 3 d) 4
- Q.2 TRIAC behaves as \_\_\_\_\_ switch (CO1)  
a) Mechanical b) Bi-Directional  
c) Unidirectional d) None of the above
- Q.3 Which power electronic device does not have a gate.  
a) IGBT b) DIAC  
c) TRIAC d) JFET
- Q.4 Triggering Techniques used for DIAC is \_\_\_\_\_. (CO1)  
a) Gate voltage triggering  
b) Gate current triggering  
c) Break over voltage triggering  
d) Break over current triggering

- Q.5 Single phase full wave half controlled bridge rectifier consist of \_\_\_\_\_ SCR. (CO4)  
 a) 1 b) 2  
 c) 3 d) 4
- Q.6 A Chopper is a (CO7)  
 a) AC to DC converter b) DC to AC converter  
 c) AC to AC converter d) DC to DC converter
- Q.7 Class-B choppers operates in \_\_\_\_\_ quadrant. (CO7)  
 a) 1st b) 2nd  
 c) 3rd d) 4th
- Q.8 AUPS with 150AH, 12V battery is connected to a 150W. What will be backup time of the UPS (CO6)  
 a) 3 hour b) 6 hour  
 c) 9 hour d) 12 hour
- Q.9 Thyristor is a \_\_\_\_\_ device. (CO2)  
 a) PNP b) PN  
 c) PNPN d) None of the above
- Q.10 Commutation used for AC drives (CO8)  
 a) Class A b) Class C  
 c) Class D d) Class F

#### SECTION-B

**Note: Objective type questions. All questions are compulsory. (10x1=10)**

- Q.11 Speed of motor \_\_\_\_\_ with the increase in firing angle of a thyristor bridge. (CO8)
- Q.12 Relationship between synchronus speed of AC drive and frequency is \_\_\_\_\_. (CO8)

- Q.13 Minimum anode current to maintain thyristor in on state is \_\_\_\_\_. (CO2)
- Q.14 Reverse saturation current of an SCR \_\_\_\_\_ (increase/decreases) with increase in gate current. (CO2)
- Q.15 SCR is a bidirectional device. (True/False) (CO1)
- Q.16 The primary source of power in Off-line UPS is battery. (True/False) (CO6)
- Q.17 Series inverter uses \_\_\_\_\_ type of commutation. (CO7)
- Q.18 IN a single phase full wave half controlled bridge rectifier a SCR conducts in both the halves of AC supply. (True/False) (CO4)
- Q.19 Average output voltage of a single phase full wave fully controlled rectifier is less than that of single phase full wave fully controlled rectifier (True/False) (CO4)
- Q.20 Dual converter circuit are designed only for three phase systems. (True/False) (CO7)

#### SECTION-C

**Note: Short answer type Question. Attempt any twelve questions out of fifteen Questions. (12x5=60)**

- Q.21 Explain gate triggering of SCR. (CO2)
- Q.22 Explain the need of heat sinks for power electronics devices. (CO2)
- Q.23 Define string efficiency. (CO2)
- Q.24 Explain the need of freewheeling diode. (CO4)
- Q.25 Explain the VI characteristics of UJT. (CO3)
- Q.26 Differentiate between series and parallel inverter. (CO7)