

- Q.31 Describe Universal Shift Register in detail with Truth Table and Logical Circuit.
- Q.32 Explain the Logic Diagram, Truth Table and Operation of Master-Slave J-K flip Flop.
- Q.33 Discuss truth table, logic diagram and logical expression of a Full Subtractor.
- Q.34 What is MUX? Design a 1 :8 MUX by using truth table logical expression and logical circuit.
- Q.35 What is Logic Gate? Draw the Symbol, Truth Table, Logical Expression of different types of logic gates.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Minimize the following Boolean expression using K-Map and realize the logic Circuit using NAND gates only.
 $F(P,Q,R,S) = \sum M(0,1,3,9,10,12,13,15) + d(2,4,6,8)$
- Q.37 What is Shift Register? Explain various types of Shift Register with the help of logic diagram and truth table. Also write down applications of shift register.
- Q.38 Explain the working of following D to A Converter with suitable diagram.
- R/2R Ladder Digital to Analog Converter
 - Binary Weighted Digital to Analog Converter

No. of Printed Pages : 4
 Roll No.

202445/122445/062445

4th Sem / Mechatronics Engineering Subject:- Digital Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 $(43)_{10} = (\dots\dots\dots)_2$
- 101011
 - 1110
 - 1100
 - 1111
- Q.2 According to associative law of multiplication
- $X(YZ) = (XY)Z$
 - $Z=XY$
 - $X+Y=Y+X$
 - None of these
- Q.3 Which equation shows a SOP expression
- $A+B(C+D)$
 - $AB+BC+A$
 - $(A+B)(C+D)$
 - None of these
- Q.4 _____ Flip Flop have Race Around Condition.
- Master Slave
 - J-K Flip-Flop
 - RS Flip-Flop
 - D Flip-Flop
- Q.5 The output of a gate is High when all the inputs are Low. This is true for
- AND
 - NAND
 - NOR
 - OR
- Q.6 Distinct digits used in Hexadecimal Number system are

- a) 0 to 7 and A to F b) 0 to 9 and A to F
 c) 0 to 8 and A to F d) 0 to 9 and A to G
- Q.7 AD-multiplexer can be used for
 a) Parallel to serial data conversion
 b) Serial to parallel data conversion
 c) Parallel to parallel data conversion
 d) None of these
- Q.8 Which gate is known as universal gate?
 a) NAND b) OR
 c) XOR d) NOT
- Q.9 How many bits are there in the Binary Number 1110000111001100
 a) 3 b) 2
 c) 16 d) 8
- Q.10 A 1 : 16 Demux has _____ output data lines
 a) 32 b) 1
 c) 16 d) None of above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define Demorgan's Theorem.
 Q.12 What is Asynchronous Counter?
 Q.13 Write any two names of A/D converter.
 Q.14 Name different types of Combinational Circuits.
 Q.15 Define Linearity.
 Q.16 $(10101101011.10110)_2 = (\dots\dots\dots\dots\dots\dots)_8$
 Q.17 Draw the symbol of NAND gate
 Q.18 What is Octal Number System?

(2) 202445/122445/062445

- Q.19 Define MOD-7 Counter.
 Q.20 Write any two application of Flip-Flop.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What is the difference between Register and Counter?
 Q.22 Subtract the following Binary Numbers:
 i) 11001-101 ii) 1100 - 10
 iii) 1100 - 1010
- Q.23 Explain Block diagram, Logical expression, Truth Table of Decimal to BCD Encoder.
 Q.24 Convert the following Hexadecimal Numbers into Binary Numbers:
 i) AF.45 ii) BCF5
 iii) 9A.23
- Q.25 What do you mean by Number System? How many number system are used in Digital electronics? Explain in detail.
 Q.26 Design Block diagram, Truth Table, Logical Expression of 3-Line-to-8-Line Decoder.
 Q.27 Differentiate between MUX and DEMUX.
 Q.28 Draw the symbol, logical expression, truth table and pulse operation of D Flip-Flop.
 Q.29 Solve the following Boolean expression:
 i) $XY + X(Y+Z) + Y(Y+Z)$
 ii) $XY(Z) + XY\bar{Z} + \bar{X}Z + X\bar{Y}Z$
- Q.30 State and explain Rules for Boolean Algebra.

(3) 202445/122445/062445