

- Q.32 How 555 timer can be used as Monostable multivibrator?
- Q.33 Explain op-amp as adder circuit.
- Q.34 Draw and explain the pin diagram of IC 555 Timer.
- Q.35 What are the disadvantages of open loop operational amplifier?

SECTION-D

Note: Long Answer type question. Attempt any two questions. (2x10=20)

- Q.36 What is a multivibrator? What are its types. Explain briefly the operation of Bistable multivibrator with the help of diagram.
- Q.37 Explain the working and construction of Wein Bridge Oscillator.
- Q.38 Write a short note on any two:-
- Piezoelectric crystal
 - Barkhausen criteria for oscillations
 - Q-Factor

No. of Printed Pages : 4

127543

Roll No.....

Branch : Fire Tech. & Safety

Subject : Electronic Devices & Circuits

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory. (10x1=10)

- Q.1 In Class A amplifier, operating point is located at ____.
- Centre of load line
 - Near saturation
 - Cut off point
 - None of the above
- Q.2 The impedance of RLC series circuit at resonance is ____.
- Resistive
 - Capacitive
 - Inductive
 - None of the above
- Q.3 Positive feedback in an amplifier ____.
- Increases the voltages gain
 - Decreases the voltage gain
 - Reduces noise
 - Increases the output impedance
- Q.4 An oscillator always needs an amplifier with ____
- Negative feedback
 - Both types of feedback
 - Positive feedback
 - An LC tank circuit
- Q.5 In parallel RLC circuit, the impedance at resonance is ____.
- Zero
 - Maximum
 - Minimum
 - None of the above

- Q.6 When RL circuit is used as differentiator output is taken across_____.
- a) Inductor b) Resistor
c) Source d) None of the above
- Q.7 The bistable multivibrator has only _____ stable state.
- a) No stable state b) One
c) Two d) None of the above
- Q.8 The efficiency of CVT is generally_____.
- a) Less than 60% b) Zero
c) More than 85% d) None of the above
- Q.9 For ideal operational amplifier, which is not its characteristics_____.
- a) Infinite open loop gains
b) Infinite bandwidth
c) Infinite output resistance
d) Zero output resistance
- Q.10 The close loop gain of inverting amplifiers is equal to _____.
- a) Open loop gain b) R_1/R_F
c) $-R_F/R_1$ d) None of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What is power amplifier?
- Q.12 Name various feedback configurations?
- Q.13 What is the efficiency of class A power amplifier?
- Q.14 What is the difference between amplifier and oscillator.

(2)

127543

- Q.15 What is the resonant frequency of RC phase shift oscillator?
- Q.16 On which pin of 555 timer, threshold is applied?
- Q.17 What is the value of impedance of RC circuit?
- Q.18 Define the term linear wave shaping circuit.
- Q.19 Define switches. What are different types of switches?
- Q.20 Draw the block diagram of inverting operational amplifier.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 How a voltage amplifier is different from power amplifier?
- Q.22 How amplifiers are divided on the basis of selection of operating point.
- Q.23 What is the effect of negative feedback on output resistance?
- Q.24 What is an oscillator? Name various types of oscillators.
- Q.25 What are the salient features of emitter follower circuit?
- Q.26 Briefly explain negative clipper diode circuit with the help of diagram.
- Q.27 Draw and explain the integrator using op-amp.
- Q.28 Explain the operation of UPS.
- Q.29 Draw and explain the working of SMPS.
- Q.30 How a transistor works as amplifier?

(3)

127543