

Q.21 List 4 difference between uncontrolled and controlled rectifiers? (CO2)

Q.22 Describe working of three phase Dual converter using suitable circuit diagram? (CO3)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

Q.23 Design a circuit for speed control of ceiling fan?
(CO4)

Q.24 Draw and explain construction, working and V-I characteristics of SCR? (CO1)

Q.25 What is chopper? List its types along with quadrant of operation? Explain class E chopper in detail? (CO3)

No. of Printed Pages : 4
Roll No.

222831/212831

3rd Sem / Automation & Robotics
Subject : Drives and Control Systems

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 SCR have _____ number of layers: (CO1)

- a) 1 b) 2
c) 3 d) 4

Q.2 ATRIAC is a _____ device: (CO3)

- a) Unidirectional b) Bidirectional
c) Tri directional d) Both a and b

Q.3 Between peak point and valley point, resistance of UJT is _____. (CO1)

- a) Positive b) Low
c) Negative d) High

Q.4 In single phase full wave full control bridge type rectifier _____ SCR are used. (CO2)

- a) 2 b) 4
c) 6 d) 3

Q.5 An inverter converts _____ into _____ (CO3)

- a) DC,AC b) AC,DC
c) DC,DC d) AC,AC

Q.6 An online UPS transfer has _____ ms transfer time. (CO5)

- a) 0 b) 5
c) 30 d) 3600

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 What is Dual Converter? (CO3)

Q.8 Expand SMPS? (CO5)

Q.9 Define dual converter? (CO3)

Q.10 SCR can pass current to load in both half cycles of the supply. (T/F) (CO1)

(2) 222831/212831

Q.11 In R-C based gate triggering circuit firing angle can be up to 180°. (T/F) (CO2)

Q.12 Define duty cycle? (CO3)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 Compare online and offline UPS? (CO5)

Q.14 What is commutation? List its types and explain any one in details? (CO1)

Q.15 Explain three phase full wave half-controlled rectifier with waveform and circuit diagram? (CO2)

Q.16 List 5 properties of the material suitable for Heat Sink? (CO1)

Q.17 Differentiate between AC and DC drives? (CO4)

Q.18 Draw and explain snubber circuit for SCR protection? (CO1)

Q.19 Define holding current and latching current? (CO1)

Q.20 Explain operation of parallel inverter with waveform and circuit diagram? (CO3)

(3) 222831/212831