

SECTION-B

Note: Objective type questions. All questions are compulsory (5x1=5)

- Q.6 A _____ signal is discrete in nature.
Q.7 A full adder can add _____ number of bits.
Q.8 A counter is a _____ circuit consisting of a combination of flip flops used for counting pulses. (Combination/Sequential)
Q.9 Full form of SISO _____
Q.10 A.A=_____

SECTION-C

Note: Short answer type questions. Attempt any six questions out of eight questions. (6x5=30)

- Q.11 Write the differences between synchronous and asynchronous counters.
Q.12 Explain De Morgan's theorem.
Q.13 Differentiate between RAM and ROM.
Q.14 Explain Half adder with circuit diagram.
Q.15 Write a short note on SSI, MSI, LSI and VLSI.
Q.16 Describe JK Flip Flop.
Q.17 Explain about encoder with block diagram.
Q.18 Discuss principle and working of seven segment display.

SECTION-D

Note: Long answer type questions. Attempt any one questions out of two questions. (1x10=10)

- Q.19 Explain in detail the working of SIPO shift register.
Q.20 What are logic gates? Explain all logic gates with symbol and Truth Table.

(100) (2) 188543

No. of Printed Pages : 2

188543

Roll No.

Level 4 / 2nd. Sem. / DVOC

Medical Imaging Tech., SD

Subject : Digital Electronics

Time : 2 Hrs.

M.M. : 50

SECTION-A

Note: Multiple-choice questions. All questions are compulsory (5x1=5)

- Q.1 The binary number 0110 1100 is of _____ bytes.
a) 1 b) 2
c) 3 d) 4
Q.2 According to boolean algebra, which of the following is valid
a) $X+X=0$ b) $1.X=X$
c) $0.X=X$ d) $X.X=1$
Q.3 The number of select lines for 1:16 DEMUX are ____
a) 2 b) 3
c) 4 d) 5
Q.4 A Decade counter has _____ states
a) 8 b) 9
c) 10 d) 11
Q.5 The NOR gate is OR Gate followed by
a) OR Gate b) AND Gate
c) NOT Gate d) NAND Gate

(1) 188543