

- c) Both d) None
- Q.6 The collector is _____ doped.
- a) Medium b) Lightly
- c) Heavily d) None
- Q.7 The efficiency of half wave rectifier is
- a) 40.6 b) 25
- c) 80.2 d) None
- Q.8 The transistor works as an amplifier in _____
- a) Active b) Saturation
- c) Cut off d) None
- Q.9 The most popular biasing method used in amplifier circuit is
- a) Fixed b) Voltage divider
- c) Emitter resistor d) None
- Q.10 JFET has _____ terminals
- a) 3 b) 2
- c) 1 d) 4

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What are active components?

(2)

170927

- Q.12 JFET stands for _____
- Q.13 Draw NPN transistor
- Q.14 Draw the symbol of LED
- Q.15 What is doping
- Q.16 What is transistor biasing ?
- Q.17 What is Q point?
- Q.18 Define intrinsic semiconductor
- Q.19 Define bandwidth
- Q.20 Write two applications of Zener diode.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Compare conductor and insulator.
- Q.22 Draw the VI characteristics of semiconductor diode and explain.
- Q.23 Explain direct coupled amplifier.
- Q.24 Explain photo diode.
- Q.25 Explain half wave rectifier circuit and its rectifier efficiency.
- Q.26 Explain the loading effect in multistage amplifier.
- Q.27 How to select an operating point.

(3)

170927