

No. of Printed Pages : 4

Roll No.

180945/170945

4th Sem / Branch : Elect.

Subject:- Digital Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 11011 in Binary is equal to _____ in Decimal.
a) 10 b) 15
c) 27 d) 50
- Q.2 The number of Digits in Hexadecimal Numbers System is
a) 8 b) 10
c) 16 d) 2
- Q.3 According to Boolean Algebra $A+1=$
a) 0 b) 2
c) -1 d) 1
- Q.4 In 8:1 MUX How many select lines are required?
a) 1 b) 2
c) 4 d) 3
- Q.5 1 Byte has _____ Number of bits
a) 8 b) 4
c) 2 d) 1

(1)

180945/170945

Q.6 ANAND GATE is AND GATE followed by

- a) NOR Gate b) NOT Gate
c) XOR Gate d) OR Gate

Q.7 A four variable K-Map has _____ cells.

- a) 4 b) 8
c) 16 d) 32

Q.8 _____ is a Universal Gate

- a) NOT b) NAND
c) OR d) XOR

Q.9 A half Adder has _____ inputs.

- a) 2 b) 3
c) 4 d) 5

Q.10 1st compliment of 111001 is

- a) 101011 b) 100011
c) 000110 d) 111001

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

Q.11 $36_{10}=(\quad)_2$

Q.12 Define A/D converter.

Q.13 Base of Octal system is _____.

Q.14 A.A= _____

Q.15 Full form of RAM is _____.

(2)

180945/170945

- Q.16 In inverter gate, if input A=1 then output 4 = ____.
- Q.17 Draw symbol of AND Gate.
- Q.18 Draw symbol of XOR Gate.
- Q.19 Convert 1111 into Hexadecimal.
- Q.20 Full form of LCD is _____.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Convert $47_{10} = ()_2 = ()_8 = ()_{16}$
- Q.22 State and prove De-morgan's Theorem.
- Q.23 Draw the truth table, symbol of AND Gate.
- Q.24 Do the subtraction using 1's complement method.
10001-1101
- Q.25 Explain difference between Analog signal and Digital signal.
- Q.26 Solve the following Boolean expression.
i) $g = \overline{AC} + \overline{ABC}$
ii) $g = (A+B)(A+C)$
- Q.27 Explain PIPO shift Register.
- Q.28 Explain T Flip Flop.
- Q.29 Discuss truth table, logic diagram and logical expression of a Half Adder.
- Q.30 Explain difference between ROM, RAM, EPROM, EEPROM.

(3)

180945/170945

- Q.31 What is De Multiplexer? Draw its block diagram and explain 1:8 Demultiplexer.
- Q.32 Describe Ring Counter in detail with Truth Table and Logical circuit.
- Q.33 Explain 7-segment Decoder.
- Q.34 Explain 7-segment display Device.
- Q.35 Draw the symbol and truth table for XOR Gate.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Simplify the function using K map $g(A,B,C,D) = \sum m(1,2,5,7,9,11,13) + \sum d(6,10,14)$
- Q.37 Draw the block diagram and explain successive Approximation Analog to Digital Converter.
- Q.38 Draw the Block Diagram and explain Binary weighted D/A converter.

(2260)

(4)

180945/170945