

- Q.26 Explain the need of stabilization of operating point.
- Q.27 Discuss transformer couplings used in multi stage transistor amplifier.
- Q.28 Differentiate N type and P type extrinsic semiconductor.
- Q.29 Draw the characteristics of zener diode and explain it.
- Q.30 Explain the concept of h-parameters of a transistor..
- Q.31 Draw the circuit of 2-stage RC coupled transistor amplifier.
- Q.32 What are the main advantages of FET over BJT.
- Q.33 Explain the working of PNP transistor.
- Q.34 Define PIV and Ripple factor. what is its value for Half wave rectifier
- Q.35 Explain N channel JFET.

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 Draw the circuit diagram of Full wave rectifier bridge and explain its working along with waveforms.
- Q.37 Classify solids on the basis of energy level diagram.
- Q.38 Draw the circuit of single stage transistor amplifier and explain it.

No. of Printed Pages : 4

120933/030933

Roll No.

3rd Sem / Electrical, GE, Power Station Engg., Elect. & Eltx. Engg., Fine Tech & Safety

Subject:- ELECTRONICS-I/ BASIC EITX

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 In case of ideal current sources, they have _____
- zero internal resistance
 - low value of voltage
 - large value of current
 - infinite internal resistance
- Q.2 Pick the incorrect statement among the following .
- Inductor is a passive element
 - Current source is an active element
 - Resistor is a passive element
 - Voltage source is a passive element
- Q.3 How does a semiconductor behave at absolute zero ?
- Conductor
 - Insulator
 - Semiconductor
 - Protection device
- Q.4 What is a Zener diode used as?
- Oscillator
 - Regulator
 - Rectifier
 - Filter

- Q.5 BJT stands for_____
- Bi-Junction Transfer
 - Blue Junction Transistor
 - Bipolar Junction Transistor
 - Base Junction Transistor
- Q.6 Which junction is forward biased when transistor is used as an amplifier ?
- Emitter-Base
 - Emitter-Collector
 - Collector-Base
 - No junction is forward biased
- Q.7 The best transistor configuration is
- CE
 - CB
 - CC
 - None
- Q.8 Faith full Amplification is obtained when the operating point of the transistor is
- near saturation
 - in the middle of the active region
 - near cutoff region
 - any of the above.
- Q.9 The frequency response of transformer coupling is _____
- Good
 - Very Good
 - Excellent
 - Poor
- Q.10 Which of the following statement is true about FET ?
- It has high output impedance
 - It has high input impedance

- It has low input impedance
- It does not offer any resistance

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 The electric components which cannot process the signal are called _____ components.
- Q.12 Define Doping.
- Q.13 Explain forbidden energy gap.
- Q.14 What is knee voltage for silicon diode.
- Q.15 Draw the symbol of PNP transistor.
- Q.16 Define operating point in transistor biasing.
- Q.17 What is AC load line.
- Q.18 Define multistage transistor Amplifier.
- Q.19 Write the full form of MOSFET.
- Q.20 What are rectifiers.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What are constant voltage sources? Draw the symbol of practical AC Voltage source.
- Q.22 Show a conversion of practical voltage source in to current source with appropriate circuit.
- Q.23 Draw the atomic structure of Germanium and Boron.
- Q.24 What are filter circuits. Explain any one filter circuit.
- Q.25 Compare the three transistor configuration (CB, CE, CC).