

- Note : Course Outcome (CO) mentioned in the question paper is for official purpose only.

a) 4                      b) 8  
c) 16                     d) 32

- Q.6 If both inputs of Ex-OR gate are 1, the output will be \_\_\_\_\_. (CO4)  
 a) 0                                      b) 1
- Q.7 The ASCII is \_\_\_\_\_ bit code. (CO2)  
 a) 5                                      b) 6  
 c) 7                                      d) 8
- Q.8 MOD 8 Counter requires \_\_\_\_\_ number of flip flops. (CO8)  
 a) 2                                      b) 4  
 c) 8                                      d) 10
- Q.9 A digital signal has \_\_\_\_\_ levels. (CO3)  
 a) 0                                      b) 1  
 c) 2                                      d) Infinite
- Q.10 8:1 Multiplexer has \_\_\_\_\_ select lines. (CO07)  
 a) 1                                      b) 2  
 c) 3                                      d) 4

### Section-B

**Note: Objective type questions. All questions are compulsory. (10x1=10)**

- Q.11 Write any two advantages of digital signals. (CO1)
- Q.12 Draw symbol of NAND gate. (CO4)
- Q.13 Expand CMOS. (CO2)
- Q.14 Convert 1010 into its 2's complement. (CO2)

- Q.15 What is base of Hexadecimal system? (CO2)
- Q.16 Define positive logic. (CO3)
- Q.17 Define Encoder. (CO7)
- Q.18 Name any one Adder IC. (CO7)
- Q.19 Expand SIPO. (CO8)
- Q.20 Define sequential circuit. (CO8)

### Section-C

**Note: Short answer type Question. Attempt any twelve questions out of fifteen Questions. (12x5=60)**

- Q.21 By taking one example, Show how error correction is performed using parity? (CO2)
- Q.22 Differentiate between TTL & CMOS logic families. (CO2)
- Q.23 Draw the truth table & logic diagram of NOR gate. (CO4)
- Q.24 Convert GRay 11001101 into Binary. (CO2)
- Q.25 Explain in brief the working of Full adder. (CO7)
- Q.26 Convert a binary number 10110101 into Hexadecimal & Octal. (CO4)
- Q.27 Explain in brief the working of BCD to 7 Segment decoder. (CO7)
- Q.28 Draw the schematic & truth table of S-R flip flop. (CO8)
- Q.29 With the help of diagram, explain PIPO shift register. (CO8)