

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

Q.23 Explain in details about Boolean rules and Law. (CO1)

Q.24 Simplify using K-map and realize the circuit with NAND gates only. (CO2)

$$Y = a_m(1,3,7,11,15) + d(0,2,5)$$

Q.25 Explain the architecture of 8051 Microcontroller. (CO4)

### 3rd Sem / Artificial Intelligence & Machine Learning

**Subject : Digital Electronics & Microcontrollers**

Time : 3 Hrs.

M.M. : 60

## SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The number of digits in octal system is (CO1)

a) 8                                      b) 9  
c) 2                                      d) 10

Q.2 A NOR gate is equivalent to an OR gate followed by  
gate (CO1)

a) OR                                      b) NOT  
c) NOR                                     d) AND

Q.3 The number of select line for 16:1 MUX are \_\_\_\_\_.  
(CO2)

a) 6                      b) 4  
c) 2                      d) 3

Q.4 A four variable K-Map has \_\_\_\_\_ cells. (CO2)

- a) 4                                      b) 8  
c) 16                                      d) 10

Q.5 A full adder circuit has outputs (CO3)

- a) 1                                      b) 2  
c) 4                                      d) 3

Q.6 How many interrupts sources are available in the 8051 microcontroller (CO4)

- a) 2                                      b) 4  
c) 5                                      d) 8

### SECTION-B

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 One's complement of 1011001 is \_\_\_\_\_ (CO1)

Q.8  $A+A=$  \_\_\_\_\_ (CO1)

Q.9 What is Associative Law? (CO2)

Q.10 4:1 MUX has \_\_\_\_\_ number of select lines. (CO3)

Q.11 A combinational circuit doesn't have \_\_\_\_\_ (CO4)

Q.12 Reset pin is usually indentified as \_\_\_\_\_ in 8051 (CO4)

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 A K-Map of three variables contains \_\_\_\_\_ cells. (CO2)

Q.14 Two's complement of 111101 is \_\_\_\_\_ (CO2)

Q.15 Write a short note on Logic gates. (CO2)

Q.16 Implement a NOR gate by using NAND gates only (CO2)

Q.17 Give the basic function of a DEMUX. Draw block diagram and Truth Table of an 1 x 8 DEMUX. (CO2)

Q.18 Explain SIPO shift register.

Q.19 Write down some application of counters (CO3)

Q.20 Why 8051 is called 8 bit Microcontroller (CO4)

Q.21 Difference between Microprocessor and Microcontroller. (CO4)

Q.22 Write difference between CISC and RISC. (CO4)