

No. of Printed Pages : 4 171041/121041/031041
Roll No.

4th Sem / Branch : Eltx, Power Eltx

**Subject:- NETWORK FILTER &
TRANSMISSION LINES**

Time : 3Hrs. M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 How many terminals a two port network has
a) 1 b) 2
c) 3 d) 4
- Q.2 A two port is reciprocal or bilateral provided
a) $Z_{11}=Z_{22}$ b) $Z_{11}=Z_{12}$
c) $Z_{12}=Z_{21}$ d) $Z_{21}=Z_{22}$
- Q.3 Characteristics impedance for asymmetrical network at both the ports is
a) Same b) Different
c) Defined d) Not defined
- Q.4 In symmetrical T network what is the value of series arm impedance
a) Z_1 b) $Z_1/2$
c) Z_2 d) $Z_2/2$
- Q.5 For a prototype LPF, the phase constant β in the attenuation band is given by _____

(1) 171041/121041/031041

- a) π b) 0
c) ∞ d) $\pi/2$

- Q.6 A band pass filter may be obtained using a high pass filter followed by
a) Low pass filter b) High pass filter
c) Band pass filter d) Band Reject filter
- Q.7 For a prototype LPF, Z_0 in attenuation band is
a) Capacitive b) Inductive
c) Resistive d) None of the above
- Q.8 Input impedance of Short circuited loss line with length $l/4$ is
a) Infinity
b) Zero
c) Characteristics impedance
d) None of the above
- Q.9 An active network has
a) an emf source b) a current source
c) Both d) None of the above
- Q.10 If $K=0$, Then VSWR will be
a) 0 b) 1
c) 2 d) All of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 A L-network is _____ network. (symmetrical /asymmetrical)

(2) 171041/121041/031041

- Q.12 A network having pairs of terminal is called two port network. (two/four)
- Q.13 Decibel is unit of admittance. (True/False)
- Q.14 An ideal filter should have.....attenuation in pass band.
- Q.15 An Attenuator amplifies the signal.(True/False)
- Q.16 Write full form of BPF
- Q.17 What is the formula for cut off frequency of LPF?
- Q.18 Define the term dielectric loss ?
- Q.19 An equivalent circuit of Transmission line has capacitance inarm.(series/shunt)
- Q.20 Write full form of VSWR.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Derive an expression for characteristic impedance of 'T' network.
- Q.22 What is asymmetrical network ? Explain iterative impedance of an asymmetrical network.
- Q.23 Differentiate between Linear and Non linear network.
- Q.24 Explain concept and significance of Iterative impedance
- Q.25 Design a symmetrical 'T' attenuator
- Q.26 What are the uses of attenuator ?
- Q.27 Draw and Derive the design equation of L-type attenuator

- Q.28 Draw and explain the characteristics(phase shift vs frequency) of T filter
- Q.29 Explain concept of band pass filter?
- Q.30 What is difference between active and passive filter? Explain in detail
- Q.31 What is a stub ? Explain the principle of impedance matching using stub.
- Q.32 A lossless line is terminated in pure resistance of 600Ω if characteristic impedance is 400Ω. Find the value of SWR.
- Q.33 Explain the concept of transmission line at high frequency
- Q.34 Write a short note on crystal filter
- Q.35 List different types of Transmission line.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Describe and explain different types of networks in detail with the help of diagrams
- Q.37 For the asymmetrical PI network having series impedance 50Ω and shunt arm impedance 150Ω and 250Ω, find the asymmetrical network properties
- Q.38 Write a short note on any two-
- Applications of Transmission Line
 - Need of m-derived filter
 - Chebyshev filter