

- Q.24 Design a full adder circuit using NAND gates only.
- Q.25 What is a D flip flop ? Discuss its applications.
- Q.26 With the help of neat sketch, Explain successive approximation A/D converter.
- Q.27 What do you understand by EPROM and PROM ? Explain
- Q.28 Why address and data bus is multiplexed in 8085 ?
- Q.29 Write a short note on Counters.
- Q.30 Explain different interrupts in 8085 microprocessor.
- Q.31 Convert  $(177.25)_{10}$  to Octal number.
- Q.32 Explain the working of R-S flip flop.
- Q.33 Simplify the expression  $(A+B)(A+C)$
- Q.34 Draw Pin diagram of 8085 microprocessor.
- Q.35 Explain with the help of necessary diagram how will you convert a digital signal to analog signal.

#### SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 Draw architecture of 8085 microprocessor and explain each block.
- Q.37 Find the minimum expression for the equation  $y = \sum m(0,1,3,4,5,7,8,11,12,15)$  using K-map.
- Q.38 Explain the working of successive approximation analog to digital converter.

No. of Printed Pages : 4                      120955-030955-105855  
Roll No. ....

**Semester : 5 th**  
**Branch : Electrical, GE. power station Engg.**  
**Subject:- Digital Electronics & Microprocessors**

Time : 3Hrs.    M.M. : 100

#### SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The value of radix in binary number system is \_\_\_\_\_
- a) 2    b) 8  
c) 10    d) 1
- Q.2 The universal gate is .....
- a) NAND gate                                      b) OR gate  
c) AND gate                                      d) None of the above
- Q.3 A single transistor can be used to build ..... gates.
- a) OR gate                                      b) NOT gate  
c) AND gate                                      d) NAND gate
- Q.4 Algebra of logic is termed as \_\_\_\_\_
- a) Numerical logic                                      b) Boolean algebra  
c) Arithmetic logic                                      d) Boolean number

- Q.5 A 3 bits full adder contains \_\_\_\_\_  
 a) 3 Combinational inputs  
 b) 4 Combinational inputs  
 c) 6 Combinational inputs  
 d) 8 Combinational inputs
- Q.6 The flip-flop is only activated by \_\_\_\_\_  
 a) Positive edge trigger  
 b) Negative edge trigger  
 c) Either positive or Negative edge trigger  
 d) Sinusoidal trigger
- Q.7 How many clock pulses do a successive approximation converter requires for obtaining a digital output.  
 a) Twelve  
 b) Six  
 c) Eight  
 d) None of the mentioned
- Q.8 Memory permits data to be stored and retrieved at comparable speed is called  
 a) R/W memory                      b) RAM memory  
 c) ROM memory                      d) EPROM memory
- Q.9 8085 microprocessor is an 8-bit microprocessor designed by ?  
 a) IBM                                      b) Dell  
 c) Intel                                      d) VAX

(2) 120955-030955-105855

- Q.10 Flag register is an 8-bit register having \_\_\_\_\_ 1 bit flip-flops  
 a) 3    b) 4  
 c) 5    d) 6

### SECTION-B

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Give any two examples of universal gate.  
 Q.12 How many bits are there in one byte \_\_\_\_\_  
 Q.13 Expand EPROM  
 Q.14 What do you mean by logic ?  
 Q.15 A Flip flop is a memory element ( True / False )  
 Q.16 A half adder can add \_\_\_\_\_ bits  
 Q.17 The radix of Decimal Number System is \_\_\_\_\_  
 Q.18 8085 microprocessor has \_\_\_\_\_ address line  
 Q.19 LED stands for \_\_\_\_\_  
 Q.20 A full Adder has three inputs and two outputs ( True / False )

### SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Convert  $(3AB)_{16}$  to decimal number.  
 Q.22 Write short note on Universal gates.  
 Q.23 State and prove De-morgan's Theorems.

(3) 120955-030955-105855