

No. of Printed Pages : 4
Roll No.

221014/212817

NEP / 1st Sem. / ECE

Subject : Fundamentals of Electrical Engg

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 Unit of current is (CO1)

- a) Volts b) Ampere
- c) Ohm d) Watt

Q.2 Watt meter is used for measuring (CO1)

- a) Energy b) Current
- c) Voltage d) Power

Q.3 An Ideal voltage source has internal Resistance (CO2)

- a) Zero b) One
- c) Infinity d) Two

(1) 221014/212817

Q.4 Unit of Impedance is (CO3)

- a) Ampere b) Ohm
- c) Watt d) Second

Q.5 Unit of Flux is (CO4)

- a) Ohm b) Webes
- c) Coulomb d) Farad

Q.6 In Lead Acid cell Positive plate is made of (CO5)

- a) Lead b) Lead oxide
- c) Copper d) Lead sulphate

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Unit of voltage is _____. (CO1)

Q.8 Unit of Resistance is _____. (CO1)

Q.9 In KCL Algebraic sum of currents meeting at a point = _____. (CO2)

Q.10 Unit of Frequency is _____. (CO3)

Q.11 Maximum value of Power factor is _____. (CO3)

Q.12 Unit of M.M.F. is _____. (CO4)

(2) 221014/212817

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Two Resistors of 3Ω and 6Ω are first connected in series and then in parallel. Find the total equivalent resistance in each case. (CO1)
- Q.14 Explain effect of temperature on the Resistance of a conductor. (CO2)
- Q.15 Explain KCL and KVL (CO2)
- Q.16 Define and explain Ohm's Law. (CO2)
- Q.17 Define Maximum Power Transfer theorem. (CO2)
- Q.18 Explain series and parallel connection of Inductors. (CO4)
- Q.19 Define and explain R.M.S. value of A.C. (CO3)
- Q.20 Draw and explain Independence Triangle in R-L series circuit. (CO3)
- Q.21 Derive the formula for power in pure Resistance (CO3)
- Q.22 Explain the Reactions that take place at Anode & Cathode during charging in lead acid cell. (CO5)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Define and explain Thevenin Theorem and Norton Theorem. (CO2)
- Q.24 Compare Electric circuit and Magnetic circuit. (CO4)
- Q.25 Explain construction, working principle and applications of Lead Acid cell. (Co5)