

SECTION-D

Note: Long answer questions. Attempt any two questions out of three Questions. (2x8=16)

- Q.23 Simplify using K-map & realize using Logic Gates. (CO2)

$$F(A, B, C, D) = \sum m(0, 2, 4, 5, 6, 7, 8, 12)$$

- Q.24 What are logic gates? Explain all logic gates with symbol and Truth Table. (CO1)

- Q.25 Explain the Architecture of 8051 microcontroller with neat and clean diagram. (CO4)

No. of Printed Pages : 4

223831

Roll No.

3rd Sem.

Branch : Artificial Intelligence & Machine Learning

Sub.: Digital Electronics & Microcontrollers

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice Questions. All Questions are compulsory. (6x1=6)

- Q.1 What are the digits used to represent binary number system? (CO1)

- a) 0 b) 0 to 8
c) 0,1 d) 0,1,2

- Q.2 The output of AND gate is low _____ . (CO1)

- a) All the time b) When any input is low
c) When any input is high d) When all inputs are high

- Q.3 In 4:1 MUX, How many select lines are required. (CO2)

- a) 4 b) 3
c) 2 d) 1

Q.4 A Half adder circuit has _____ inputs. (CO3)

- a) 2 b) 3
c) 4 d) 8

Q.5 A flip flop has _____ stable states. (CO3)

- a) 1 b) 2
c) 3 d) 4

Q.6 How many timers exist in 8051? (CO4)

- a) 1 b) 2
c) 3 d) 4

SECTION-B

Note: Objective/Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Write any two advantages of digital signal over analog signal. (CO1)

Q.8 Draw the symbol of AND Gate. (CO1)

Q.9 1's complement of 11101 is _____. (CO1)

Q.10 A combinational circuit doesn't have _____. (CO3)

Q.11 What is the size of ROM in 8051 microcontroller. (CO4)

Q.12 $A + AB =$ _____. (CO2)

SECTION-C

Note: Short answer type Questions. Attempt any eight questions out of ten Questions. (8x4=32)

Q.13 Solve using 2's complement method. (CO1)

100111

- 10011

Q.14 Convert $(1001011)_2 = (?)_8 = (?)_{16}$. (CO1)

Q.15 Write the operation of PIPO shift register. (CO3)

Q.16 Solve using Boolean algebra. (CO1)

$$Y = A + \overline{A}BC + ABC + AB\overline{C} = A\overline{C}$$

Q.17 Write a short note on Decoder circuit. (CO2)

Q.18 Explain Half Adder with diagram. (CO3)

Q.19 Differentiate between Latch and Flip Flop. (CO2)

Q.20 Explain T Flip Flop.

Q.21 Difference between Microprocessor and Microcontroller. (CO4)

Q.22 Write a short note on SFRs of 8051 microcontroller. (CO4)