

- Q.31 Explain the application of an OPAMP as differentiator.
- Q.32 Write a short note on IC555.
- Q.33 Write short note on CVT.
- Q.34 Describe duty cycle.
- Q.35 What is a regulated power supply?

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 Explain the operation of Wein Bridge Oscillator with a neat circuit diagram.
- Q.37 i) Explain the operation of RC circuit as an integrator.
ii) Explain the circuit of a Bistable Multivibrator.
- Q.38 Explain the construction and working of a Push Amplifier. What are its advantages?

No. of Printed Pages : 4

Roll No.

120943

**4th Sem / Branch : Elect, Power Station Engg.,
Elect. & Eltx. Engg.
Subject:- Electronics-II**

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The push pull circuit must use _____ operation.
a) Class A b) Class C
c) Class B d) Class AB
- Q.2 Reasonance occurs in an LC circuit when
a) $X_L \gg X_C$ b) $X_L \ll X_C$
c) $X_L = X_C$ d) None of the above
- Q.3 At series resonance the circuit behaves as _____ load.
a) Capacitive b) Resistive
c) Inductive d) None of the above
- Q.4 At parallel resonance the circuit offers _____ impedance.
a) Zero b) Minimum
c) Maximum d) None of the above
- Q.5 The negative feedback in an amplifier _____ the voltage gain.
a) Reduces b) Increases
c) Does not change d) Produces oscillations

- Q.6 A bistable multivibrator has
 a) One stable state
 b) Two stable state
 c) No stable state
 d) The state can't be changed
- Q.7 Time constant of RC circuit is
 a) RC
 b) C/R
 c) R/C
 d) Independent of R and C
- Q.8 A switch has _____ states.
 a) One b) Zero
 c) Three d) Two
- Q.9 Zener diode used in a power supply.
 a) Is forward Biased b) Is reversed biased
 c) Rectifies the input d) Filters the input
- Q.10 An ideal OP-AMP has
 a) Infinite voltage gain
 b) Infinite input resistance
 c) Zero output resistance
 d) All of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Complementary push pull amplifiers use _____ & _____ transistors.
- Q.12 At resonance a parallel tuned circuit offers _____ impedance.

(2)

120943

- Q.13 Tuned voltage amplifiers are used to amplify _____ frequencies.
- Q.14 What is the value of gain provided by an emitter follower circuit?
- Q.15 Oscillators use _____ type of feedback.
- Q.16 In a transistor oscillator active device is _____.
- Q.17 Write full form of UPS.
- Q.18 Output voltage of a 7805 IC voltage regulator is _____ Volts.
- Q.19 The integrator circuit is _____ pass filter.
- Q.20 Ideal OP AMP has _____ input impedance.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 How does an oscillator produce output signal without any input?
- Q.22 What is heat sink? Why it is used in Power Amplifiers?
- Q.23 Explain the concept of parallel resonance.
- Q.24 Explain the differences between Class A and Class B amplifiers.
- Q.25 Explain Astable Multivibrator circuit.
- Q.26 Explain the working of transistor as a switch.
- Q.27 Explain the concept of load regulation.
- Q.28 What is the concept of negative feedback?
- Q.29 What are the applications of electronic oscillators?
- Q.30 Define clamping. Draw a clamping circuit.

(3)

120943