

No. of Printed Pages : 4  
Roll No. ....

180945/170945

**4th Sem. Branch: Electrical Engg.**  
**Sub : Digital Electronics**

Time : 3 Hrs.

M.M. : 100

**SECTION-A**

**Note: Multiple choice Questions. All Questions are compulsory. (10x1=10)**

- Q.1 What is the radix of Octal Number System?  
a) 8                                      b) 16  
c) 2                                        d) 6
- Q.2 Convert  $(312)_8$  into decimal Number?  
a)  $(201)_{10}$                               b)  $(202)_{10}$   
c)  $(203)_{10}$                               d)  $(204)_{10}$
- Q.3 The ones complement of 11011 binary is?  
a) 00111                                  b) 11100  
c) 00100                                  d) 11000
- Q.4  $a + \bar{a}$  is equal to ?  
a) 0                                        b) 4  
c) 3                                        d) 1
- Q.5 A Half adder has :  
a) 3 inputs & 2 outputs    b) 2 inputs & 2 outputs  
c) 1 inputs & 2 outputs    d) 2 inputs & 1 outputs

(1)

180945/170945

- Q.6 What is the standard form of S-R flip flop?  
a) Set Reset                              b) Single reset  
c) Simple Reset                          d) None of the above
- Q.7 An inverter output is the complement of its input. (True/False)
- Q.8 There are \_\_\_\_\_ cells in a 4-variable K-map.  
a) 12                                        b) 16  
c) 18                                        d) 8
- Q.9 What is a shift register?  
a) An adder circuit  
b) A memory circuit  
c) A combinational circuit  
d) A decoder circuit
- Q.10 The memory in which the stored data is lost, when power is switched off is?  
a) ROM                                      b) RAM  
c) PROM                                    d) Ferrite Core Memory

**Section-B**

**Note: Objective type questions. All questions are compulsory. (10x1=10)**

- Q.11 Convert Binary Number 1100110 into Octal number?
- Q.12 Draw the standard symbol of R-S flip-flop.
- Q.13 Define half adder?

(2)

180945/170945

- Q.14 Define encoder?
- Q.15 Write one the use of multiplexer?
- Q.16 Expand LED & LCD.
- Q.17 Define T flip flop.
- Q.18 What is the use of A/D Converters.
- Q.19 Draw the symbols for OR gate with two inputs.
- Q.20 Who invented Boolean Algebra?

### Section-C

**Note: Short answer type Questions. Attempt any twelve questions out of fifteen Questions. (12x5=60)**

- Q.21 Explain NAND gate?
- Q.22 Explain Full adder with diagram?
- Q.23 Convert  $(76)_{10}$  to its equivalent Binary and  $(11100110.110)_2$  to its equivalent Decimal?
- Q.24 Differentiate between RAM & ROM?
- Q.25 Differentiate synchronous & asynchronous counter?
- Q.26 State the De Morgan's theorems?
- Q.27 Differentiate between Digital & Analog signals.
- Q.28 What is meant by K-Map? Also draw two variable K-Map?
- Q.29 What are the basic Logic gates? Also draw the symbols of basic logic gates?

(3)

180945/170945

- Q.30 State the Distributive Law of Boolean Algebra with example?
- Q.31 Explain the operation of D flip flop with diagrams?
- Q.32 Compare Differentiate between POS & SOP?
- Q.33 Draw the truth table of  $(xy) = \bar{x} + y$ .
- Q.34 Describe the working of serial In and serial out shift register?
- Q.35 Differentiate between Combinational Circuits and Sequential Circuits?

### Section-D

**Note: Long answer questions. Attempt any two questions out of three Questions. (2x10=20)**

- Q.36 Minimize the following expression by using K-map.  
 $F(A, B, C, D) = \sum (0, 1, 2, 5, 7, 13, 14) + d(3, 6, 9)$
- Q.37 Explain J-K Flip Flop. Discuss any five Applications of the Flip Flops.
- Q.38 Explain the followings  
 i) 2's Complement method  
 ii) Merits of Semiconductor Memory

(2220)

(4)

180945/170945