

120926

**2nd Sem / Elect. Power Stat. Engg., Elect& Eltx Engg
/ Fire Tech & Safety**

Time : 3Hrs.

M.M. : 100

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.5 Average emf of Nickle & Cadmium cell is

- a) 1.0 V b) 1.2 V
c) 1.8 V d) 2.0 V

- Q.6** The ideal voltage source should have

- a) Large value of emf
- b) Small value of emf
- c) Zero source resistance
- d) Infinite source resistance

- Q.7 Which of the system is four wire system:

- a) Delta b) Star
c) Both star and delta d) None

- Q.8 An ideal current source has

- Zero internal resistance
- High internal resistance
- Infinite internal resistance
- Very low internal resistance

- Q.9 The eddy current loss in the transformer is reduced by

- a) Reducing the resistance of core
- b) Using laminated core
- c) Both A & B correct
- d) Not possible of reduce

- Q.10 The area hysteresis loop is a measure of

- Permittivity
- Susceptance
- Energy loss per cycle
- Magnetic Flux

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Unit of voltage is_____.
- Q.12 Two resistance of value 10 ohm & 20 ohm are connected in parallel, what is the total equivalent resistance of the parallel combination_____?
- Q.13 Unit of flux is_____?
- Q.14 Power consumed in pure inductive circuit is zero. (True/False)
- Q.15 In star connection, line voltage $V(L)=$
- Q.16 Define magnetic flux.
- Q.17 Form factor of Sinusoidal wave is_____.
- Q.18 Write any one primary cell.
- Q.19 Define peak factor.
- Q.20 State Ohm's law.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain advantages of electrical energy over other forms of energy.
- Q.22 Explain inductances in series and parallel.
- Q.23 Compare a magnetic circuit with an electric circuit.
- Q.24 State and explain Superposition theorem with example.
- Q.25 Draw the circuit diagram to measure voltage, current, power and energy in an AC circuit.
- Q.26 Explain Faraday's law of electromagnetic induction.

(3)

120926

- Q.27 State and explain ohm's law.
- Q.28 Explain Active power, reactive power and apparent power.
- Q.29 Derive an expression for the force on a current carrying conductor placed in a magnetic field.
- Q.30 What are the advantages of 3-phase system over 1-phase system.
- Q.31 Find the expression for energy stored in an inductor.
- Q.32 Write short note on j-notation and its application.
- Q.33 Differentiate between A.C. and D.C.
- Q.34 Write a short note on care and maintenance of lead acid batteries.
- Q.35 What is power factor and what are the disadvantages of low power factor?

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain principle, construction and applications of lead acid batteries.
- Q.37 Write short note on any two:
 - a) 3-phase balanced and unbalanced circuits.
 - b) Practical importance of power factor.
 - c) Energy stored in a magnetic field.
- Q.38 Compare star and delta connection of 3-phase connection and derive relationship between phase voltage & line voltage, phase current & line current in star and delta connections?

(1060)

(4)

120926