

4th Sem, **Branch** : Electrical Engg.**Subject** : Digital Electronics**Time** : 3 Hrs.**M.M.** : 100**SECTION-A****Note** : Multiple choice questions. All questions are compulsory. (10x1=10)

- Q.1 A byte is a string of _____ bits.
 a) 2 b) 6
 c) 8 d) 4
- Q.2 A NAND gate is equivalent to an AND gate followed by _____ gate.
 a) XOR b) NOT
 c) OR d) NOR
- Q.3 If $A=0$ and $B=0$ then $A.B.$ = _____
 a) 0 b) 1
 c) 10 d) 11
- Q.4 The number of select lines for 8:1 MUX are _____
 a) 3 b) 5
 c) 4 d) 2
- Q.5 A full adder can add _____ number of bits.
 a) 1 b) 4
 c) 3 d) 4

Q.6 If $J=0$ and $K=1$ then the output Q = _____.

- a) 1 b) 0
 c) No change d) Toggle

Q.7 A 4 Variable K map has _____ cells.

- a) 9 b) 16
 c) 8 d) 3

Q.8 Expand LCD

- a) Light Cell Device
 b) Liquid Crystal Display
 c) Light Crystal display
 d) None of these

Q.9 $A+1$ =

- a) A b) 1
 c) 0 d) A.1

Q.10 The universal gate is _____.

- a) NAND b) OR
 c) AND d) NOT

SECTION-B**Note** : Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Convert binary number 11011 into decimal number.
- Q.12 Define Encoder.
- Q.13 Draw the symbol of NAND Gate.
- Q.14 Define Min Term.

- Q.15 Write Down Full Form of PISO.
- Q.16 Define Latch.
- Q.17 What is the 1's complement of 11001011.
- Q.18 Write the name of any one type of D/A converter.
- Q.19 Expand RAM.
- Q.20 The number of inputs in Half adder are?

SECTION-C

Note : Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain NAND gate as universal gate.
- Q.22 Draw and explain circuit diagram of 8:1 MUX.
- Q.23 Explain Half adder with circuit diagram.
- Q.24 Explain S-R Flip Flop with diagram.
- Q.25 Explain K map and its advantage.
- Q.26 Write any five difference between Static RAM and Dynamic RAM.
- Q.27 Explain Decoder with block diagram.
- Q.28 Explain R/2R D/A converter.
- Q.29 Explain SISO with block diagram.
- Q.30 Write five applications of Flip-Flop?
- Q.31 Convert $(124)_{10}$ and $(100100)_8$ into binary number.
- Q.32 Explain Synchronous Counter.
- Q.33 Explain DeMorgan's Theorems.
- Q.34 Explain NOR gate with truth table.
- Q.35 Do Subtraction using 2's Complement method:
 $(11011)_2 - (01101)_2$

SECTION-D

Note : Long Answer type question. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Minimize the following expression by using K map and realize the result by using NAND gates $Y = f(m(1, 3, 7, 11, 15) + d(0, 2, 5))$
- Q.37 Explain Master Slave J - K Flip Flop in detail.
- Q.38 Explain the working of Ramp type analog to digital convertor with circuit diagram.