

No. of Printed Pages : 4  
Roll No. ....

180962/170962

**6<sup>th</sup> Sem / Elect.**

**Subject:- Industrial Electronics and Control of Drives**

Time : 3Hrs.

M.M. : 100

**SECTION-A**

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The number of gates in a silicon controlled switch is (CO-1)
- a) One                                      b) Two  
c) Three                                    d) Four
- Q.2 To turn off an SCR, it is necessary to reduce its current to less than (CO-1)
- a) Trigger current                      b) Holding current  
c) Breakover current                  d) None of the above
- Q.3 A UJT has..... (CO-2)
- a) Two pn junctions                  b) One pn junction  
c) Three pn junctions                d) None of the above
- Q.4 A fully controlled converter uses (CO-3)
- a) Diodes only                            b) Thyristors only  
c) Both diodes and thyristors  
d) None of the mentioned

- Q.5 In a three-phase half wave 6-pulse mid-point type diode rectifier, each diode conducts for (CO-3)
- a) 120°                                      b) 90°  
c) 60°                                        d) 180°
- Q.6 An inverter converts (CO-4)
- a) dc into variable dc                  b) ac into dc  
c) dc into ac  
d) ac into ac of different frequency
- Q.7 Choppers is a (CO-4)
- a) AC-DC converters                  b) AC-AC converters  
c) DC-AC converters                  d) DC-DC converters
- Q.8 A Cycloconverter can be .
- a) Step down                              b) Step up  
c) Step down or Step up                d) Neither of the above
- Q.9 Armature control method is used in d.c. motor to get (CO-6)
- a) Constant Speed  
b) Speeds above normal speed  
c) Speeds below normal speed  
d) Both B & C
- Q.10 SMPS is used for \_\_\_\_\_ (CO-7)
- a) Obtaining controlled ac power supply  
b) Obtaining controlled dc power supply  
c) Storage of dc power  
d) Switch from one source to another

## SECTION-B

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 A TRIAC can be triggered by gate pulse of \_\_\_\_\_ polarity. (CO-2)
- Q.12 The process of turning OFF a thyristor is called \_\_\_\_\_. (CO-1)
- Q.13 The series inverter uses \_\_\_\_\_ type of commutation. (CO-4)
- Q.14 In half wave rectifiers; one switching device is used. (True/False) (CO-3)
- Q.15 Cycloconverters are used for generating high frequencies. (True/False) (CO-4)
- Q.16 A UJT has \_\_\_\_\_ PN Junction. (CO-2)
- Q.17 The duty cycle of a chopper is expressed as \_\_\_\_\_. (CO-5)
- Q.18 Armature control method is used in d.c. motors to get speed below \_\_\_\_\_. (CO-6)
- Q.19 DC motors provide \_\_\_\_\_ starting torque. (CO-6)
- Q.20 UPS stands for \_\_\_\_\_. (CO-7)

## SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Draw and explain the circuit of single phase half controlled full wave rectifier. (CO-2)
- Q.22 Draw and explain illumination control circuit using SCR. (CO-1)
- Q.23 Differentiate between controlled and uncontrolled rectifiers. (CO-3)
- Q.24 Write any five applications of thyristor converters. (CO-3)
- Q.25 Draw and explain the parallel inverter. (CO-4)
- Q.26 Explain the principle of cycloconverters ? What are its applications? (CO-5)

- Q.27 Draw a circuit for a fan regulator using a TRIAC-DIAC pair (CO-2).
- Q.28 Differentiate between On line and Off-line UPS (CO-7).
- Q.29 Explain the working principle of chopper circuit, (CO-5)
- Q.30 Explain variable voltage variable frequency method for speed control of 3-phase induction motor. (CO-6)
- Q.31 Write any five instructions for maintenance and care of lead acid batteries. (CO-7)
- Q.32 Show the basic construction of a UJT. What is its intrinsic stand off ratio ? (CO-2)
- Q.33 Compare two modes of dual converter. (CO-6)
- Q.34 Compare AC and DC drives. (CO-6)
- Q.35 What is UPS ? What are the applications of UPS system ? (CO-7)

## SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Write short technical notes on any two: (CO-2)
- (a) Construction of SCR
- (b) UJT as relaxation oscillator
- (c) TRIAC
- Q.37 What are the two main methods of speed control of d.c. separately excited motor? Explain any one in detail using circuit and block diagram. (CO-6)
- Q.38 What is inversion process ? Name different types of inverters. Explain any one with the help of circuit diagram and waveforms. (CO-4)