

No. of Printed Pages : 4 180832/170832/120832/
Roll No. 030832/031034/106544

**3rd Sem. / Comp. IT, Eltx, EI, Med. Eltx, Power
Eltx,. Elect & Eltx. Engg.**

Subject : Digital Electronics/Digital Eltx. I

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice Questions. All questions are compulsory (10x1=10)

Q.1 NOT gate has _____ input.

- a) 3 b) 2
- c) 1 d) 4

Q.2 Base/Radix of Hexadecimal number system is _____.

- a) 10 b) 8
- c) 2 d) 16

Q.3 Output of EX-OR gate is _____ when both of its inputs are HIGH.

- a) 1 b) 0
- c) Invalid d) None of the above

Q.4 A dual group in K-maps eliminates _____ number of variables.

- a) 2 b) 4
- c) 3 d) 1

Q.5 A full adder has _____ inputs.

- a) 2 b) 3
- c) 4 d) 5

Q.6 A 1:8 demultiplexer has _____ output lines.

- a) 2 b) 3
- c) 4 d) 8

Q.7 A universal shift register is a _____ circuit.

- a) Sequential b) Combinational
- c) Both A and B d) None of these above

Q.8 If $S = 0$ & $R = 1$ then the output (Q) of S-R flip flop is _____.

- a) 1 b) 0
- c) Invalid d) None of the above

Q.9 Decade counter has _____ states.

- a) 5 b) 9
- c) 4 d) 10

Q.10 The full form of ALU is _____

- a) Adder Logic Unit
- b) Arithmetic Logic Unit
- c) Add Loop unit
- d) All of these

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Give any one advantage of digital signal over analog signal.
- Q.12 Draw the symbol and truth table of EX-OR Gate.
- Q.13 State De-Morgan's Theorem.
- Q.14 Give a truth tables of 4:1 multiplexer.
- Q.15 Full Form of EPROM is _____.
- Q.16 Write any one advantage of the flip flop over the latch.
- Q.17 Explain the mode number (Modulus) in the counter.
- Q.18 Expand TTL.
- Q.19 Give the IC number of 4-bit ALU.
- Q.20 Define Accuracy in DAC

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions.

(12x5=60)

- Q.21 Differentiate between Analog signal and digital signal.
- Q.22 Convert $(6A8C)_{16}$ Hexadecimal number into binary number.
- Q.23 Explain 3-bit. Excess-3, code and Gray code.
- Q.24 Explain the NOR gate as a universal logic gate.

(3) 180832/170832/120832/
030832/031034/106544

- Q.25 Explain the Full adder with circuit diagram.
- Q.26 Define 8:1 multiplexer.
- Q.27 Explain Decimal to BCD Encoder.
- Q.28 Subtract 0101 from 1101 using 2's complement method of subtraction.
- Q.29 What is race around condition in J-K flip flop?
- Q.30 Differentiate between latch and flip flop.
- Q.31 Explain synchronous counter.
- Q.32 Explain Concept of weighted & non weighted codes.
- Q.33 Explain ALU in detail.
- Q.34 Give symbol and truth table of Sr-flip and JK - flip flop.
- Q.35 Explain Half adder.

SECTION-D

Note: Long answer type questions. Attempt any two out of three questions. (2x10=20)

- Q.36 Simplify with the help of K-MAP $f(A, B, C, D) = \sum m = (0, 2, 3, 6, 8, 10, 12, 15) + d(4, 11, 14)$ and realize the expression using NAND gates.
- Q.37 Explain R/2R ladder digital to analog converter with neat diagrams.
- Q.38 Write a short note on any two of the following:
 - a) Ring counter
 - b) Dynamic RAM,
 - c) D-flip flop

(3440)

(4) 180832/170832/120832/
030832/031034/106544