

No. of Printed Pages : 4
Roll No.

180933/170933

3rd Sem / Electrical
Subject:- Electronics II

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 In class A amplifier, collector current flows for _____
a) Less than half cycle b) Half the cycle
c) Entire cycle d) Less than entire cycle
- Q.2 Gain of emitter follower circuit is _____.
a) Unity b) Infinite
c) 10 d) 100
- Q.3 The bistable multivibrator has _____ stable state
a) One b) Two
c) No d) None
- Q.4 555 timer consists of _____
a) Comparator b) RS Flip flop
c) Transistor & resistor d) All above

Q.5 Push Pull amplifier use

- a) Class A b) Class B
c) Class C d) Class ABC

Q.6 For ideal OPAMP, value of term CMRR is _____

- a) Zero b) Infinite
c) 100 d) None

Q.7 Crystal have a very _____

- a) Low Q b) High Q
c) Small Inductance d) High Inductance

Q.8 The impedance of RLC series circuit at resonance is _____

- a) Resistive b) Capacitive
c) Inductive d) None of these

Q.9 In class A Amplifier, operating point is located at _____

- a) Centre of load line b) Near saturation
c) Cut off point d) None

Q.10 The distortion is minimum in _____ type of amplifier.

- a) Push Pull b) Class A
c) Class B d) None

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 In power amplifier _____ coupling is used?
- Q.12 Amplifiers use _____ feedback.
- Q.13 With negative feedback, the bandwidth of an amplifier _____
- Q.14 What is a tuned amplifier.
- Q.15 LC circuit is called _____.
- Q.16 Integrator circuit is a _____ filter?
- Q.17 What is clamping circuit.
- Q.18 What is a monostable multivibrator.
- Q.19 A 555 timer is 8 pin IC. (True/False)
- Q.20 An OPAMP has _____ number of inputs.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain the term: Slew rate and PSRR.
- Q.22 Write a brief note on Emitter follower circuit.
- Q.23 Explain in brief operation of Push Pull amplifier.
- Q.24 Write a note on feedback and its importance.

- Q.25 Explain working of Wien Bridge Oscillator.
- Q.26 Difference between oscillator and alternator.
- Q.27 Give applications of tuned voltage amplifiers.
- Q.28 Explain impedance matching in power amplifiers?
- Q.29 Explain the term distortion and dissipation capability.
- Q.30 Explain working of Astable multivibrator?
- Q.31 Explain the differential amplifier.
- Q.32 Explain the parallel resonance.
- Q.33 Explain transistor as a switch.
- Q.34 Write a note on CVTs
- Q.35 Discuss the effect of negative feedback on gain, stability and bandwidth

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain working of Class A ended amplifier and its collector efficiency.
- Q.37 Explain various Diode Clamping circuits.
- Q.38 Explain working of RC oscillator circuit.