

- Q.29 What is the effect of temperature on the operating point of transistors?
- Q.30 What is a dc load line? What its importance?
- Q.31 Discuss the working of single stage amplifier in CE configuration.
- Q.32 What is the need of multistage amplifiers?
- Q.33 Deduce the relation for calculating voltage gain of a 3 stages multistage amplifier.
- Q.34 Explain the working of JFET
- Q.35 Compare BJT and JFET.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain the working principle of 2 stage RC coupled amplifiers. Also draw its frequency response.
- Q.37 Explain with diagram the working of full wave bridge rectifier.
- Q.38 Write short note on any two of the following:-
- Tunnel Diode
 - Clipper Circuits
 - Rectifier Efficiency

No. of Printed Pages : 4

120933/030933

Roll No.

3rd Sem / Electrical, GE, Power Station Engg. Elect. & Elxt. Engg., Fire Tech & Safety Subject:- Electronics I/Basic Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 At absolute zero temperature, an intrinsic semiconductor
- Has excess of holes
 - Has few electrons and holes
 - Behaves like a conductor
 - Behaves like an insulator
- Q.2 The value of forbidden energy gap in semiconductors is of the order of.....
- 1 eV
 - 5 eV
 - 0 eV
 - More than 5 eV
- Q.3 The number of diodes required in a bridge rectifier circuit is/are
- one
 - two
 - three
 - four
- Q.4 The value of ripple factor for half wave rectifier is.....
- 1.21
 - 1.12
 - 0.48
 - None of these
- Q.5 The most heavily doped region in a transistor is.....
- Emitter
 - base

- c) collector d) both a) and b)
- Q.6 The advantage of selecting the Q-point in the middle of active region is that.....
- It gives better stability
 - The circuit needs a small dc voltage
 - The biasing circuit then needs less components
 - It gives distortion less output
- Q.7 The gain stability of an amplifier circuit can be improved by using
- Positive feedback
 - Negative feedback
 - Both positive and negative feedback
 - None of these
- Q.8 The purpose of coupling capacitor in an amplifier is to.....
- Match the impedance
 - Control frequency
 - Prevent dc mixing with output
 - Limit the bandwidth
- Q.9 The operations of JFET involves.....
- A flow of minority carriers
 - A flow of majority carriers
 - Recombination
 - Negative Resistance
- Q.10 What is the full form of MOSFET?
- Metal dioxide semiconductor field effect transistor
 - None of these
 - Metal oxide semiconductor field effect transformer
 - Metal oxide semiconductor field effect transistor

SECTION-B

Note: Objective type questions. All questions are compulsory.
(10x1=10)

- Q.11 What is active component? Name any two active components.
- Q.12 What is drift current?
- Q.13 How an extrinsic semiconductor is made?
- Q.14 What is a filter circuit?
- Q.15 What is the value of knee voltage of silicon diode?
- Q.16 Define the term “current gain”.
- Q.17 What is the value of ripple factor of full wave rectifier?
- Q.18 What is the principle of Photodiode?
- Q.19 Why the stabilization of operating point is needed?
- Q.20 What is JFET?

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Draw and explain the atomic structure of P-type Semiconductor.
- Q.22 Discuss the energy band diagram of semiconductor material.
- Q.23 Explain V-I characteristics of P-N junction diode?
- Q.24 Write a short note of Varactor diode.
- Q.25 Explain the working of half wave rectifier with suitable waveforms.
- Q.26 Discuss how PNP transistor works in Active Region?
- Q.27 Deduce the relation between α , β and Y .
- Q.28 Explain the various mechanism of achieving breakdown in a diode.