

No. of Printed Pages : 4  
Roll No. .... 180832/170832/120832/  
030832/031034/106544

**3rd Sem / Branch : Comp, IT, Eltx, EI,  
Med.Eltx, Power Eltx, Elect & Eltx. Engg.  
Subject:- Digital Electronics / Digital Eltx-I**

Time : 3Hrs. M.M. : 100

## SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The number of digits in Hexa decimal system is (CO2)  
a) 8 b) 10  
c) 16 d) 2
- Q.2 The NAND gate is AND gate followed by (CO4)  
a) Not Gate b) OR Gate  
c) NOR Gate d) EXOR Gate
- Q.3 In 8:1 MUX, How many select lines are required, (CO7)  
a) 4 b) 3  
c) 2 d) 1
- Q.4 JK Flip Flop consists of \_\_\_\_\_ inputs (CO8)  
a) 3 b) 4  
c) 8 d) 2
- Q.5 The binary number 11001 is equivalent to decimal number (CO2)  
a) 25 b) 24  
c) 27 d) 26

(1) 180832/170832/120832/  
030832/031034/10654

- Q.6 A Full adder circuit has \_\_\_\_\_ inputs (CO6)  
a) 2                                      b) 3  
c) 4                                      d) 8
- Q.7 \_\_\_\_\_ is universal Gate. (CO4)  
a) NAND                                b) AND  
c) OR                                     d) NOT
- Q.8 A Flip Flop stores \_\_\_\_\_ bit of information (CO8)  
a) Two                                    b) Three  
c) Four                                  d) One
- Q.9 There are \_\_\_\_\_ cells in 4-variable K-Map (CO5)  
a) 8                                        b) 16  
c) 4                                        d) 12
- Q.10 Which of the following memories must be refreshed many times per second, (CO12)  
a) EPROM  
b) ROM  
c) Dynamic Ram  
d) EEPROM

## SECTION-B

**Note:** Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 BCD code of  $(35)_{10}$  is \_\_\_\_\_ (CO3)  
 Q.12 Full form of CMOS \_\_\_\_\_ (CO4)  
 Q.13 I'S Complement of 1011001 is \_\_\_\_\_ (CO3)  
 Q.14 Full form of EPROM \_\_\_\_\_ (CO12)

(2) 180832/170832/120832/  
030832/031034/106544

- Q.15 Draw truth table of NAND Gate (CO4)  
 Q.16 Full form of ALU \_\_\_\_\_  
 Q.17 Draw truth table of sr Flip Flop. (CO8)  
 Q.18 Write any two advantages of digital signal over analog signal (CO1)  
 Q.19 Full Form of PIPO \_\_\_\_\_ (CO10)  
 Q.20 State Demorgan's theorem (CO4)

### SECTION-C

**Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain NAND gate as Universal Gate. (CO4)  
 Q.22 Explain JK Flip Flop (CO8)  
 Q.23 Convert  $(72)_{10} = (?)_2 = (?)_8$  (CO2)  
 Q.24 Explain 1:4 Demux with diagram (CO7)  
 Q.25 Subtract 1010 from 1100 using one's complement method. (CO3)  
 Q.26 Differentiate between synchronous and Asynchronous Counter (CO9)  
 Q.27 Explain D Latch with diagram (CO8)  
 Q.28 Explain SIPO Shift register (CO10)  
 Q.29 Explain Dynamic RAM. (CO12)  
 Q.30 Explain any one type of Encoder (CO7)  
 Q.31 Explain Half Adder with diagram (CO6)

- Q.32 Explain R/2R ladder network digital to analog converter. (CO11)  
 Q.33 Convert  $(35)_8 = (?)_2 = (?)_{16}$  (CO2)  
 Q.34 Explain error detection (CO3)  
 Q.35 Simplify (CO5)  
 $y = ABC + \bar{A}BC + A\bar{B}C + AC$

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Simplify using k-Map. & realize using NAND Gates only (CO5)  
 $F(A,B,C,D) = \sum m(1,2,5,7,9,11,13) + d(6,10,14)$   
 Q.37 Explain with block diagram, the working of Asynchronous Decode Counter (CO9)  
 Q.38 Explain with diagram, the working of Dual Slope A/D converter (CO11)