

3rd Sem / Branch :Elect. & Eltx. Engg.

Subject:- Fundamentals of Digital Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- | | | |
|-----|--|---------|
| Q.1 | A full adder can add _____ number of bits. | (CO-6) |
| a) | 1 | b) 3 |
| c) | 2 | d) 4 |
| Q.2 | The number of select lines for 8:1 MUX are | (CO-7) |
| a) | 3 | b) 2 |
| c) | 1 | d) 4 |
| Q.3 | A four variable K-map has _____ cells. | (CO-5) |
| a) | 32 | b) 4 |
| c) | 16 | d) 8 |
| Q.4 | Which gate is also called as universal gate? | (CO-4) |
| a) | EX-OR | b) OR |
| c) | AND | d) NAND |
| Q.5 | $A.A =$ _____ | (CO-5) |
| a) | 1 | b) 0 |
| c) | A | d) 01 |
| Q.6 | 1's complement of 1011 is | (CO-2) |
| a) | 1010 | b) 0100 |
| c) | 0111 | d) 1001 |

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain with diagram, the working of synchronous decade counter. (CO-9)
- Q.37 Explain with diagram, the working of Binary weighted D/A converter. (CO-11)
- Q.38 Minimize the following boolean expansion using K-map method. (CO-5)

$$f(A,B,C,D)=\text{am}(0,1,2,4,5,6,10,12,14)$$

- Q.7 How many flip flops are required to make a MOD-16 counter? (CO-8)
 a) 6 b) 5
 c) 3 d) 4
- Q.8 How is a JK FF mode to toggle? (CO-8)
 a) J=0, K=0 b) J=1, K=1
 c) J=1, K=0 d) J=0, K=1
- Q.9 Convert Hexadecimal value 16 to decimal (CO-2)
 a) 16 b) 22
 c) 20 d) 10
- Q.10 Shift register is a combination of _____ (CO-10)
 a) Flip flop b) Latch
 c) Encoder d) Decoder

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 CMOS stands for _____ (CO-4)
 Q.12 PIPO stands for _____ (CO-10)
 Q.13 $A+A=$ _____ (CO-5)
 Q.14 2's complement of 101101 is _____ (CO-2)
 Q.15 A NAND gate is basically a _____ gate followed by _____ gate. (CO-4)
 Q.16 16:1 MUX has _____ number of select lines. (CO-7)
 Q.17 BCD stands for _____ (CO-)
 Q.18 ASCII stands for _____ (CO-3)
 Q.19 $1011 + 1101 =$ _____ (CO-6)
 Q.20 VLSI dtands for _____ (CO-4)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Compare Analog system with digital system. (CO-1)
 Q.22 Convert $(65)_{10}=(?)_2=(?)_8$. (CO-2)
 Q.23 Convert Binary number 101101 into Gray code. (CO-2)
 Q.24 Explain NOR gate as universal gate. (CO-4)
 Q.25 Explain half adder with circuit diagram. (CO-6)
 Q.26 Explain 7-segment decoder. (CO-7)
 Q.27 Explain Rs flip flop with truth table. (CO-8)
 Q.28 What do you mean modulus of a counter? (CO-9)
 Q.29 Explain 1:4 Demultiplexer. (CO-7)
 Q.30 Explain PISO shift register. (CO-10)
 Q.31 Explain applications of A/D converter. (CO-11)
 Q.32 Explain tristate buffer register. (CO-10)
 Q.33 Explain SISO shift register. (CO-10)
 Q.34 Explain EX OR gate with truth table. (CO-4)
 Q.35 Explain De Morgan's theorem. (CO-5)