

## Time : 3 Hrs.

M.M. : 60

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

a) 8                      b) 10  
c) 16                     d) 2

a) Not Gate                      b) OR Gate  
c) NOR Gate                    d) EXOR Gate

a) 4                                      b) 3  
c) 2                                      d) 1

a) 2                                      b) 3  
c) 4                                      d) 8

Q.5 A Flip Flop stores \_\_\_\_\_ bit of information (CO3)

- a) Two                                      b) Three  
c) Four                                      d) One

Q.6 8051 is a \_\_\_\_\_ bit microcontroller. (CO5)

- a) 8    b) 16  
c) 4    d) 32s

### SECTION-B

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Write any two advantages of digital signal over analog signal (CO1)

Q.8 Draw the symbol of NOR Gate (CO1)

Q.9 1'S Complement of 1011001 is \_\_\_\_\_ (CO1)

Q.10 Full form of SIPO \_\_\_\_\_ (CO3)

Q.11 What is the size of RAM in 8051 microcontroller? (CO5)

Q.12 A K-map of three variables contains \_\_\_\_\_ cells. (CO2)

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 Convert  $(70)_{10} = (?)_2 = (?)_8$  (CO1)

(2)

223831

Q.14 Subtract 1010 from 1100 using one's complement method. (CO1)

Q.15 Explain NAND gate as Universal Gate. (CO1)

Q.16 Explain DeMorgan's Theorem. (CO1)

Q.17 Write a short note on 4:1 MUX. (CO2)

Q.18 Explain Half Adder with diagram. (CO3)

Q.19 Differentiate between asynchronous and synchronous counter. (CO2)

Q.20 Explain JK Flip Flop. (CO3)

Q.21 Draw pin diagram of 8051 microcontroller. (CO5)

Q.22 Write a short note on SFR of 8051 microcontroller. (CO5)

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

Q.23 Simplify using k-Map. & realize using NAND Gates only. (CO2)

$$F(A,B,C,D) = \sum m(2,3,4,5,7,11,12,13,15) + \sum d(6,10,14)$$

Q.24 Explain SISO Shift register in detail with the help of neat diagram. (CO3)

Q.25 Explain the block diagram of 8051 microcontroller. (CO5)

(3)

223831