

No. of Printed Pages : 4 181031/171031/121031
Roll No. /031031

**3rd Sem / Eltx, Mechatronics, Med. Eltx, Elect. &
Eltx. Engg, Power Eltx.**

Subject:- Electronic Devices and Circuits / Analog Eltx-II

Time : 3Hrs. M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The best frequency response is of _____ coupling
a) RC b) Transformer
c) Direct d) None
- Q.2 Class _____ operation gives the maximum distortion.
a) A b) C
c) AB d) None
- Q.3 Pin number 5 in timer 555 IC is _____.
a) Control voltage b) Threshold
c) Output d) reset
- Q.4 Circuit which consist of a quasi-stable state is called _____.
a) Monostable b) Bistable
c) Astable d) None
- Q.5 The common-mode gain of an op-amp is _____.
a) Very high b) Very low
c) unity d) Unpredictable

(1) 181031/171031/121031
/031031

Q.6 _____ multivibrators are used as flip-flop in digital circuits.

- a) Astable b) Monostable
c) Bistable d) None

Q.7 What is PSRR value of an ideal op-amp ?

- a) Zero b) Infinte
c) Unity d) None

Q.8 The voltage gain of a tuned amplifier is _____ at resonant frequency

- a) Minimum b) Maximum
c) average d) Zero

Q.9 The _____ is defined as the time the output is active divided by the total period of the output signal.

- a) Off time b) Active ratio
c) Duty cycle d) None

Q.10 OPAMP amplifies _____

- a) Ac only
b) Dc only
c) AC and DC
d) None

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

Q.11 CMRR stands for _____?

Q.12 What is a multistage amplifier?

(2) 181031/171031/121031
/031031

- Q.13 _____ multi vibrator is called one shot multi vibrator ?
- Q.14 PSRR stands for _____.
- Q.15 What is negative feedback.
- Q.16 What is heat sink ?
- Q.17 What is voltage amplifier.
- Q.18 The negative feedback increases _____ in amplifier .
- Q.19 An oscillator converts _____ ?
- Q.20 The multivibrator which generates square wave of its own is the _____ multivibrator.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain working of Hartley oscillator
- Q.22 Explain feedback and its type
- Q.23 Explain in brief operation DC amplifier and its frequency response.
- Q.24 Discuss the effect of negative feedback on gain, distortion and bandwidth.
- Q.25 Explain importance of impedance matching in amplifiers.

(3) 181031/171031/121031
/031031

- Q.26 Explain working of class AB amplifier
- Q.27 Explain Double tuned voltage amplifier
- Q.28 Explain concept of DC power supply?
- Q.29 Explain OP AMP as differentiator and integrator
- Q.30 Explain working of Monostable multivibrator?
- Q.31 Explain IC voltage regulator 7805
- Q.32 Explain series resonant circuit
- Q.33 Define slew rate and input offset current.
- Q.34 Explain working principle of crystal oscillator.
- Q.35 Difference between voltage and power amplifiers

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain block diagram of IC 555 and its working and applications.
- Q.37 Explain RC coupled amplifier with emitter by pass capacitor.
- Q.38 Explain heat dissipation curve and push pull amplifier.

(1460)

(4) 181031/171031/121031
/031031