

**Subject : Electronics Devices and Circuits - 1**

M.M. : 60

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 Atomic number of silicon is  
a) 12                                  b) 14  
c) 16                                  d) 32
- Q.2 Bridge rectifier uses \_\_\_\_\_ no. of diodes  
a) 1                                      b) 2  
c) 4                                      d) 8
- Q.3 The commonly used configuration of transistor is \_\_\_\_\_  
a) CB                                    b) CC  
c) CE
- Q.4 In biasing circuit, the bypass capacitor \_\_\_\_\_  
a) reduces the voltage gain  
b) increases the voltage gain  
c) stabilizes the Q point  
d) causes thermal runaway

- Q.5 An amplifier has input voltage of 20 mv, gives 2 v output, its voltage gain will be\_\_\_\_\_
- a) 40                                      b) 80  
c) 100                                      d) 1000
- Q.6 FET is a \_\_\_\_\_ controlled device.
- a) Voltage                                      b) Current  
c) Power                                      d) Both a and b

### SECTION-B

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 Give an example of pentavalent impurity.
- Q.8 Define static resistance of diode.
- Q.9 Draw symbol of NPN transistor.
- Q.10 Define ripple factor.
- Q.11 Define thermal runaway.
- Q.12 What is the full form of MOSFET?

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 How temperature affects intrinsic semiconductors?
- Q.14 Differentiate between drift & diffusion current.
- Q.15 Draw & explain a positive clipper circuit.

- Q.16 Write the mechanism of current flow in transistor.
- Q.17 Draw & explain the output CE characteristics.
- Q.18 Define biasing, why it is needed in transistors?
- Q.19 What are the factors which affect the operating point?
- Q.20 Compare the features of BJT & FET.
- Q.21 Show how DC load line is drawn?
- Q.22 Draw & explain the characteristics of JFET.

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain in detail the working of bridge rectifier circuit.
- Q.24 Draw the energy band diagram of metals, insulators & semiconductors.
- Q.25 Explain the operation of single stage amplifier.